

Single Stage Amplifiers

- ***Basic Concepts***
- ***Common Source Stage***
- ***Source Follower***
- ***Common Gate Stage***
- ***Cascode Stage***

Hassan Aboushady
University of Paris VI

References

- **B. Razavi, “Design of Analog CMOS Integrated Circuits”, McGraw-Hill, 2001.**

Single Stage Amplifiers

- *Basic Concepts*
- *Common Source Stage*
- *Source Follower*
- *Common Gate Stage*
- *Cascode Stage*

*Hassan Aboushady
University of Paris VI*

Basic Concepts I

- **Amplification is an essential function in most analog circuits !**
- **Why do we amplify a signal ?**
 - **The signal is too small to drive a load**
 - **To overcome the noise of a subsequent stage**
 - **Amplification plays a critical role in feedback systems**

In this lecture:

- **Low frequency behavior of single stage CMOS amplifiers:**
 - **Common Source, Common Gate, Source Follower, ...**
- **Large and small signal analysis.**
- **We begin with a simple model and gradually add 2nd order effects**

➔ Understand basic building blocks for more complex systems.

Approximation of a nonlinear system


Input-Output Characteristic of a nonlinear system

$$y(t) \approx \alpha_0 + \alpha_1 x(t) + \alpha_2 x^2(t) + \dots + \alpha_n x^n(t) \quad x_1 \leq x \leq x_2$$


In a sufficiently narrow range:

$$y(t) \approx \alpha_0 + \alpha_1 x(t)$$

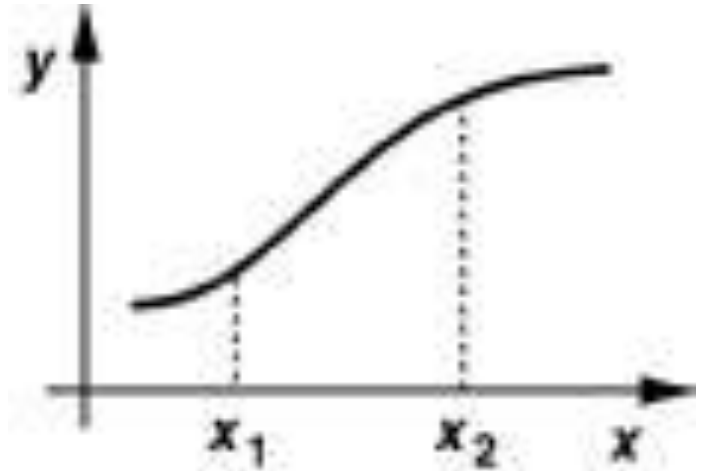where α_0 can be considered the operating (bias) point and α_1 the small signal gain



Analog Design Octagon

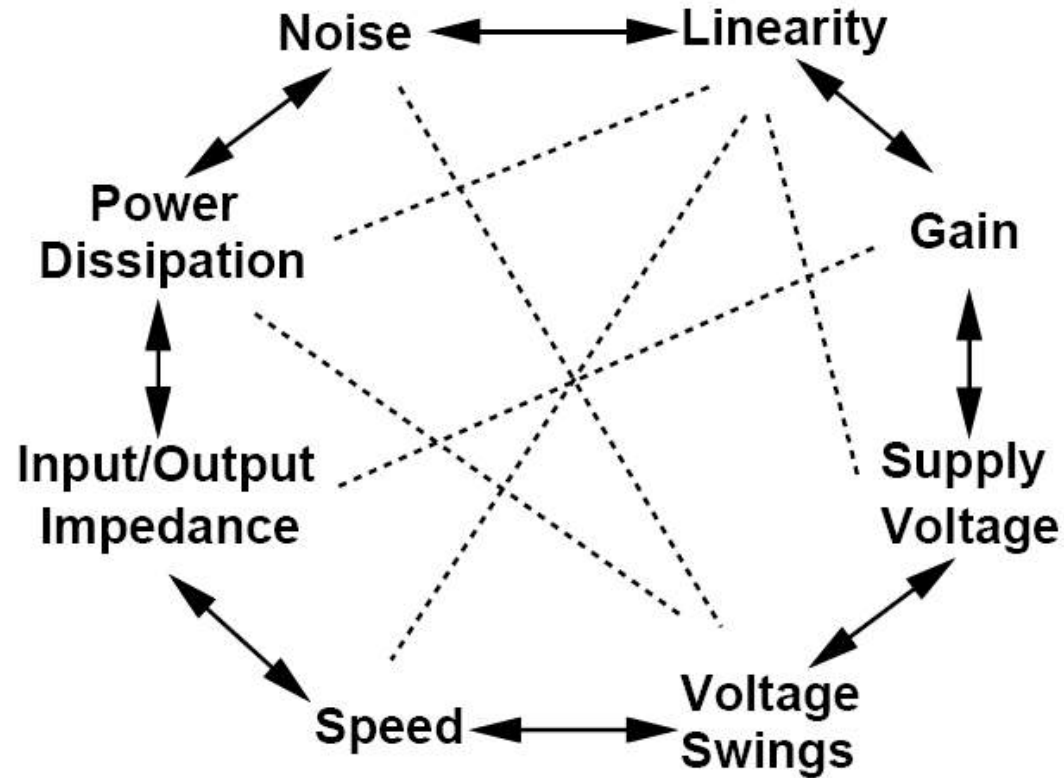



Single Stage Amplifiers

- *Basic Concepts*
- *Common Source Stage*
- *Source Follower*
- *Common Gate Stage*
- *Cascode Stage*

Hassan Aboushady
University of Paris VI

Taking Channel Length Modulation into account

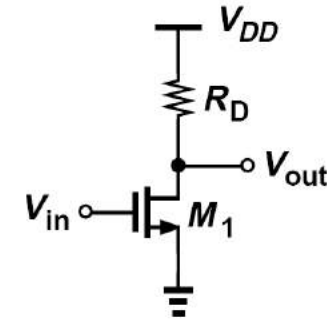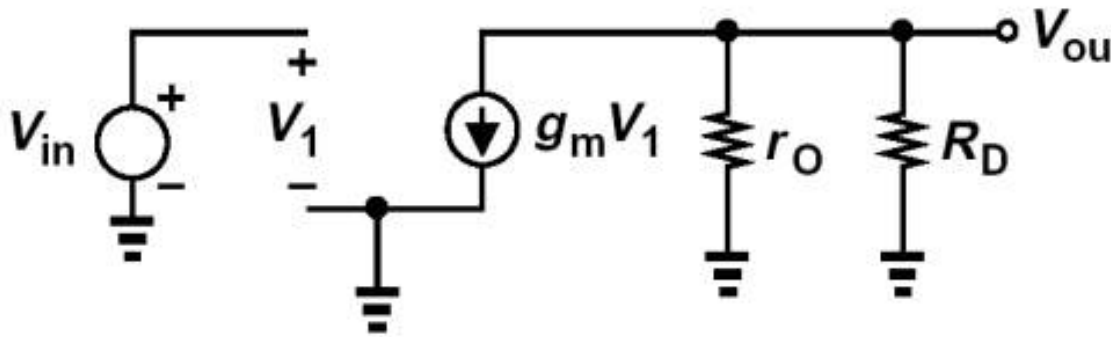Calculating A_v , starting from the Small Signal model:




(a)

..

$$\left. \begin{aligned} g_m V_1 (r_o // R_D) &= -V_{out} \\ V_1 &= V_{in} \end{aligned} \right\} \boxed{A_v = \frac{V_{out}}{V_{in}} = -g_m (r_o // R_D)}$$

CS Stage with Current-Source Load

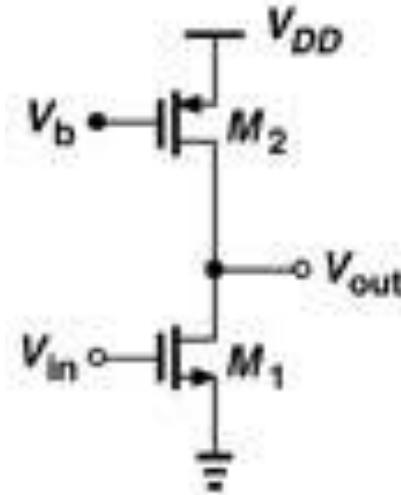- Both transistors operate in the saturation region:




$$A_v = -g_m (r_{O1} // r_{O2})$$

General expression to calculate A_v by inspection


Lemma:

$$A_v = -G_m R_{out}$$

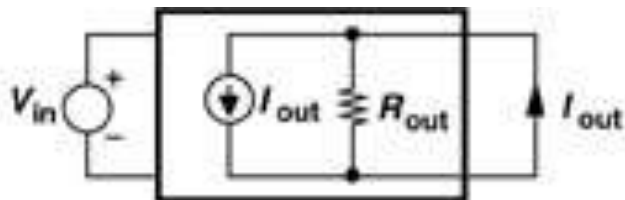
G_m : the transconductance of the circuit when the output is shorted to grounded.



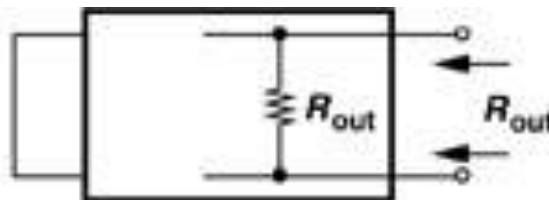
R_{out} : the output resistance of the circuit when the input voltage is set to zero.



CS with Source Degeneration

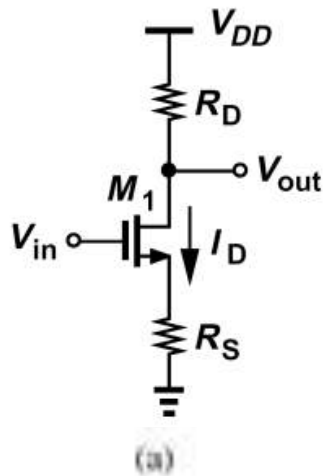

Small Signal model:

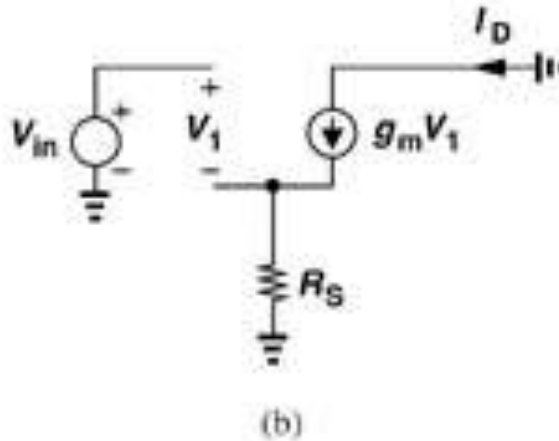

$$G_m = \frac{I_D}{V_{in}} = \frac{g_m V_1}{V_1 + g_m V_1 R_S}$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

$$A_v = -G_m R_D$$




$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

Voltage Gain of Degenerated CS

Small Signal model including body effect & channel length modulation:

$$I_{R_D} = I_{R_S} = \frac{-V_{out}}{R_D}$$
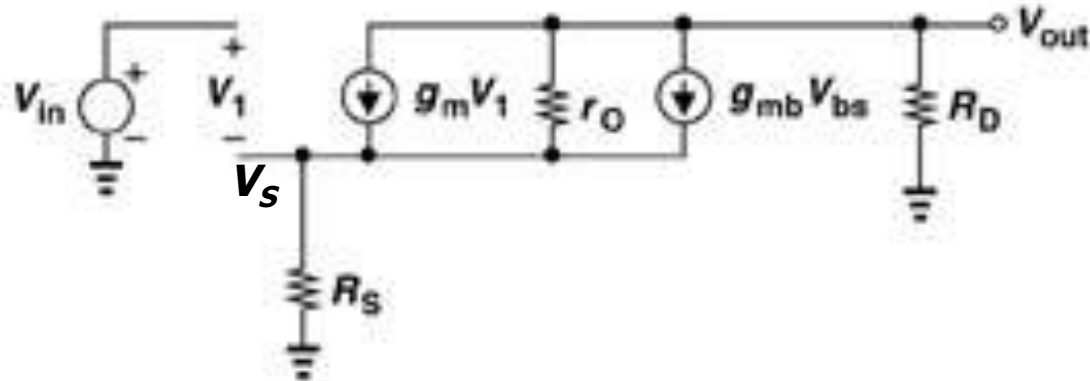
$$\Rightarrow V_S = -V_{out} \frac{R_S}{R_D}$$



The current through r_o :
$$I_{r_o} = -\frac{V_{out}}{R_D} - (g_m V_1 + g_{mb} V_{BS})$$


$$I_{r_o} = -\frac{V_{out}}{R_D} - \left[g_m \left(V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] \quad \Rightarrow \quad V_{out} = I_{r_o} r_o - \frac{V_{out}}{R_D} R_S$$

$$V_{out} = -\frac{V_{out}}{R_D} r_o - \left[g_m \left(V_{in} + V_{out} \frac{R_S}{R_D} \right) + g_{mb} V_{out} \frac{R_S}{R_D} \right] r_o - V_{out} \frac{R_S}{R_D}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -\frac{g_m r_o R_D}{R_D + R_S + r_o + (g_m + g_{mb}) R_S r_o}}$$

Gm of Degenerated CS

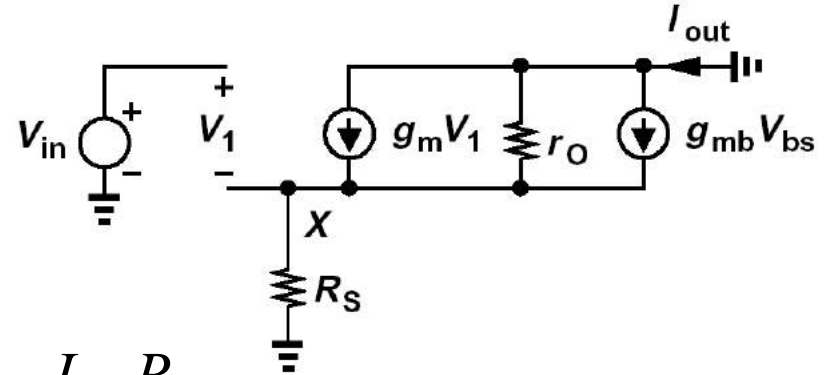Small Signal model including body effect and channel length modulation:



$$I_{out} = g_m V_1 - g_{mb} V_X - \frac{V_X}{r_o}$$

$$= g_m (V_{in} - I_{out} R_S) + g_{mb} (-I_{out} R_S) - \frac{I_{out} R_S}{r_o}$$


$$\Rightarrow G_m = \frac{I_{out}}{V_{in}} = \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$

Output Resistance of Degenerated CS

$$V_1 = -I_X R_S$$

The current flowing in r_o :
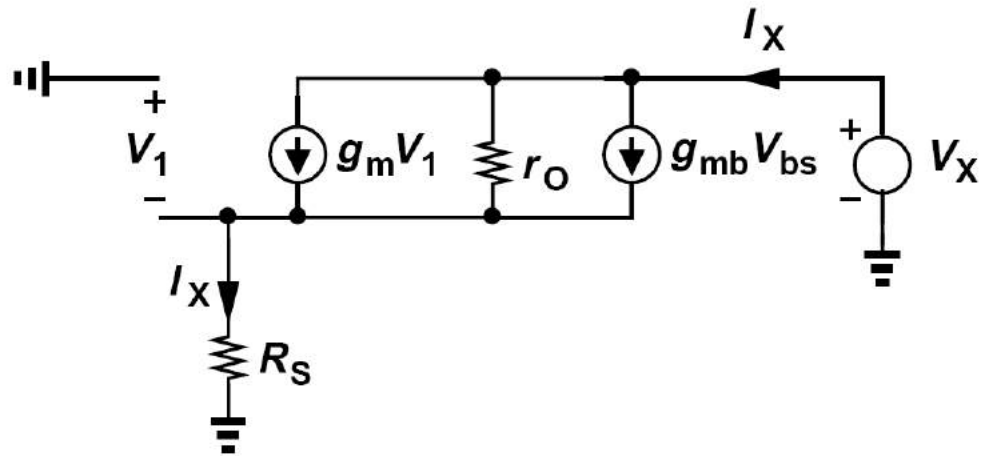
$$\begin{aligned} & I_X - (g_m + g_{mb})V_1 \\ &= I_X + (g_m + g_{mb})R_S I_X \end{aligned}$$



$$\Rightarrow V_X = r_o [I_X + (g_m + g_{mb})R_S I_X] + I_X R_S$$

$$R_{out} = \frac{V_X}{I_X} = r_o [1 + (g_m + g_{mb})R_S] + R_S$$

$$R_{out} = [1 + (g_m + g_{mb})r_o]R_S + r_o$$

$$R_{out} \approx (g_m + g_{mb})r_o R_S + r_o$$




$$R_{out} = [1 + (g_m + g_{mb})R_S]r_o$$

Single Stage Amplifiers

- *Basic Concepts*
- *Common Source Stage*
- *Source Follower*
- *Common Gate Stage*
- *Cascode Stage*

*Hassan Aboushady
University of Paris VI*

Source Follower Voltage Gain

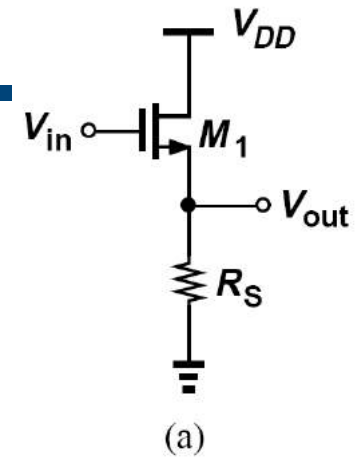

$$V_{out} = [g_m V_1 + g_{mb} V_{BS}] R_S$$

$$= [g_m (V_{in} - V_{out}) - g_{mb} V_{out}] R_S$$



$$\Rightarrow Av = \frac{V_{out}}{V_{in}} = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

Since: $g_{mb} = \eta g_m$

And for : $g_m R_S \gg 1$

$$\Rightarrow Av \approx \frac{1}{1 + \eta}$$

Small Signal Equivalent Circuit

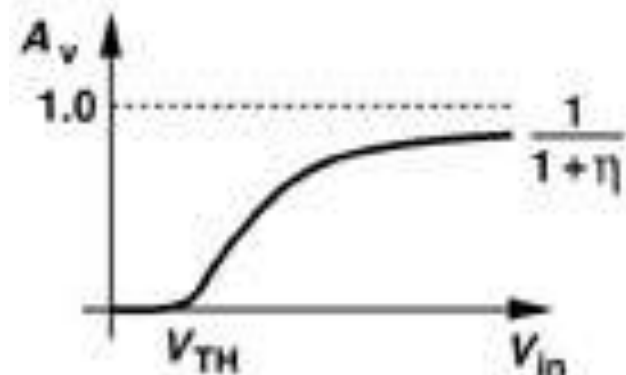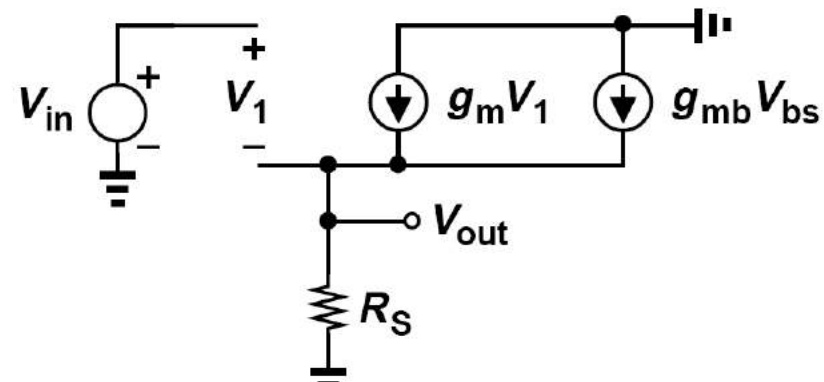



Single Stage Amplifiers

- *Basic Concepts*
- *Common Source Stage*
- *Source Follower*
- *Common Gate Stage*
- *Cascode Stage*

Hassan Aboushady
University of Paris VI

Common Gate Gain

Small Signal Signal Equivalent Circuit

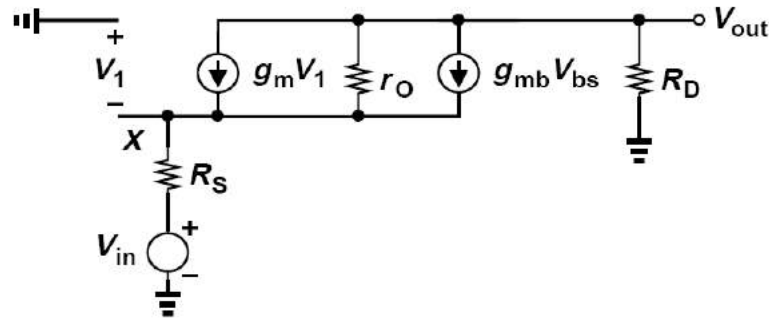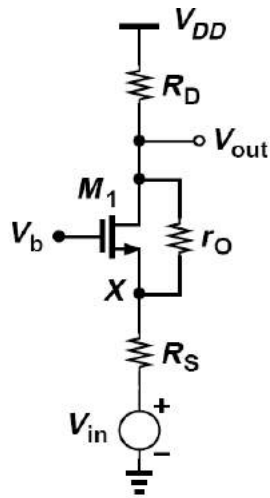

The current through R_S is equal to $-V_{out}/R_D$: $V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$

The current through r_O is equal to $-V_{out}/R_D - g_m V_1 - g_{mb} V_1$:

$$r_O \left(\frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

$$r_O \left[\frac{-V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \frac{R_S}{R_D} - V_{in} \right) \right] - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out}$$

Common Gate Gain

Common Gate Amplifier:

$$A_{vCG} = \frac{(g_m + g_{mb})r_O + 1}{R_D + R_S + r_O + (g_m + g_{mb})r_O R_S} R_D$$

Degenerated Common Source Amplifier:

$$A_{vCS} = - \frac{g_m r_O}{R_D + R_S + r_O + (g_m + g_{mb})r_O R_S} R_D$$

Single Stage Amplifiers

- *Basic Concepts*
- *Common Source Stage*
- *Source Follower*
- *Common Gate Stage*
- *Cascode Stage*

*Hassan Aboushady
University of Paris VI*

Biasing of a Cascode Stage

The cascade of CS stage and a CG stage is called “cascode”.

M1 : the input device

M2 : the cascode device

Biasing conditions:

• **M1 in saturation:**

$$V_X = V_b - V_{GS2}$$



$$V_b - V_{GS2} \geq V_{in} - V_{TH1}$$

$$V_b \geq V_{in} + V_{GS2} - V_{TH1}$$

• **M2 in saturation:**

$$V_{out} - V_X \geq V_b - V_X - V_{TH2}$$
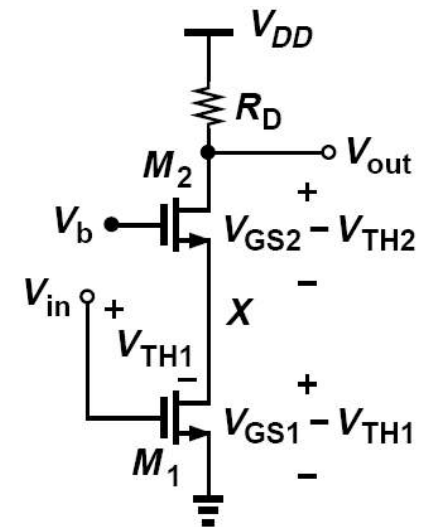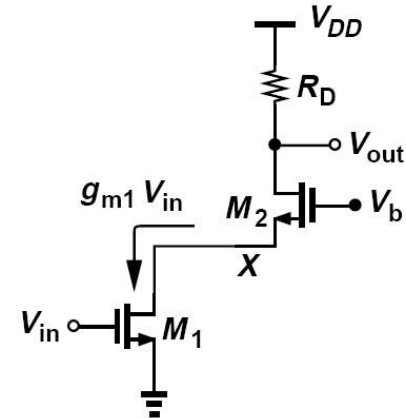
$$V_{out} \geq V_{in} - V_{TH1} + V_{GS2} - V_{TH2}$$




Cascode Stage Characteristics

Large signal behavior:

As V_{in} goes from zero to V_{DD}
 For $V_{in} < V_{TH}$ M1 and M2 are OFF

→ $V_{out} = V_{DD}$

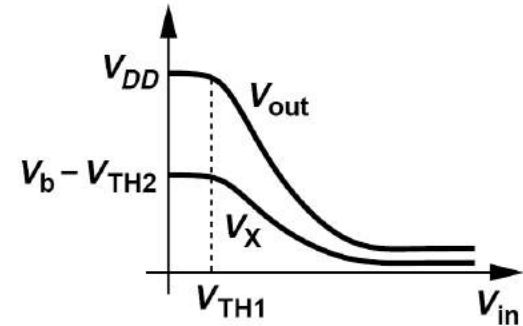

Output Resistance:



- Same common source stage with a degeneration resistor equal to r_{O1}

$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}]r_{O1} + r_{O2}$$

$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$

- M2 boosts the output impedance of M1 by a factor of $g_m r_{O2}$

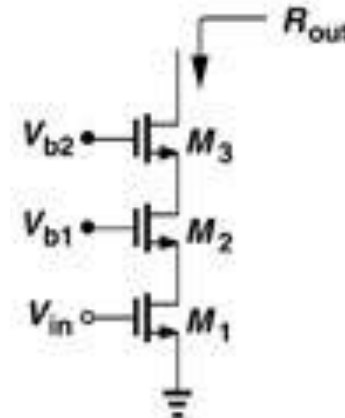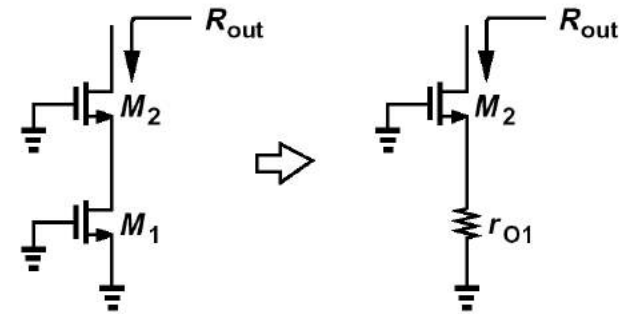- Triple cascode $R_{out} \uparrow \uparrow$
 → difficult biasing at low supply voltage.



Cascode Stage Voltage Gain


$$A_v = -G_m R_{out}$$

$$G_m \approx g_{m1}$$

Ideal Current Source:

$$R_{out} \approx (g_{m2} + g_{mb2})r_{O2}r_{O1}$$

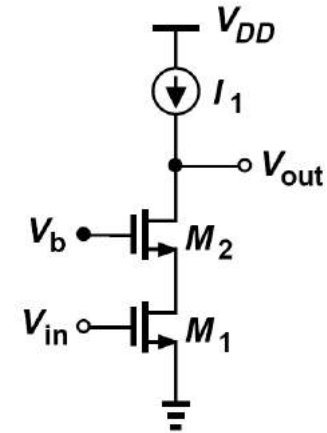
$$A_v \approx (g_{m2} + g_{mb2})r_{O2} g_{m1}r_{O1}$$




Cascode Current Source:

$$R_{out} \approx g_{m2}r_{O2}r_{O1} // g_{m3}r_{O3}r_{O4}$$

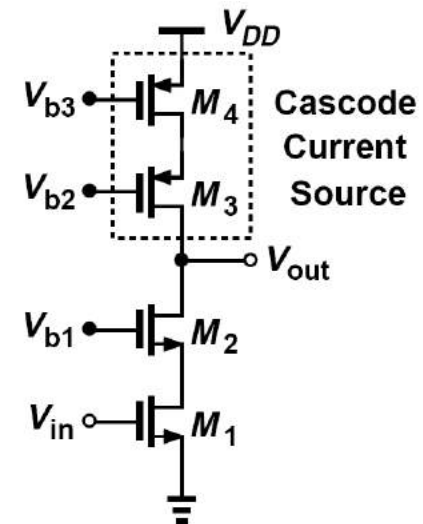
$$A_v \approx g_{m1} (g_{m2}r_{O2}r_{O1} // g_{m3}r_{O3}r_{O4})$$




Folded Cascode

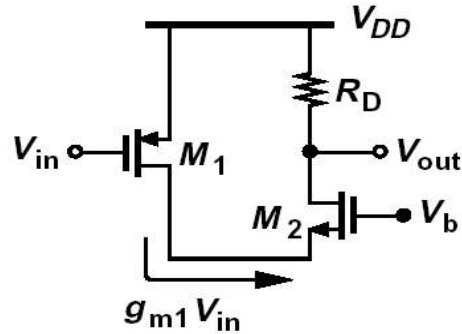

Simple Folded Cascode

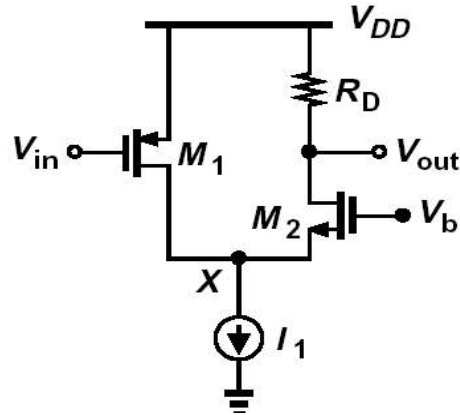

Folded Cascode with biasing

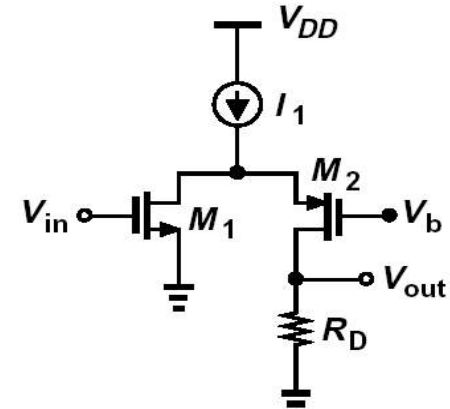


Folded Cascode with NMOS input

Output Resistance of Folded Cascode

Degenerated Common Source Stage:
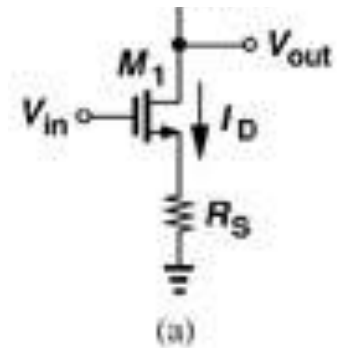
$$R_{out} = [1 + (g_{m1} + g_{mb1})r_{O1}]R_S + r_{O1}$$




Folded Cascode Stage:

M_1 → M_2

R_S → $r_{O1} // r_{O3}$
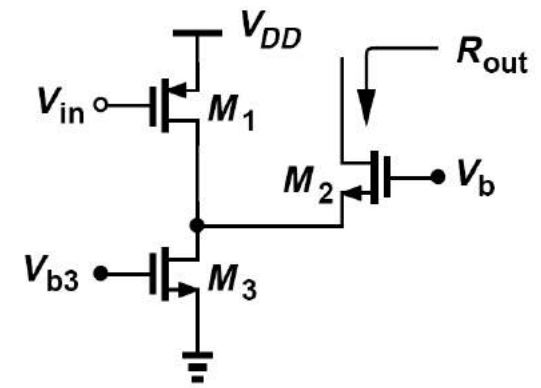
$$R_{out} = [1 + (g_{m2} + g_{mb2})r_{O2}](r_{O1} // r_{O3}) + r_{O2}$$



Voltage Gain of Degenerated CS

$$\frac{V_{out}}{V_{in}} = - \frac{g_m r_O R_D}{R_D + R_S + r_O + (g_m + g_{mb}) R_S r_O}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m r_O}{R_S + [1 + (g_m + g_{mb}) R_S] r_O} \frac{R_D [R_S + r_O + (g_m + g_{mb}) R_S r_O]}{R_D + R_S + r_O + (g_m + g_{mb}) R_S r_O}$$

$$\frac{V_{out}}{V_{in}} = G_m (R_{out} // R_D)$$

**The output resistance
of a degenerated CS stage:**

$$R_{out} = [1 + (g_m + g_{mb}) R_S] r_O$$


**The Transconductance
of a degenerated CS stage:**

$$G_m = \frac{I_{out}}{V_{in}} = \frac{g_m r_O}{R_S + [1 + (g_m + g_{mb}) R_S] r_O}$$

Estimating Gain by Inspection



$$A_v = -\frac{g_m R_D}{1 + g_m R_S} = -\frac{R_D}{1/g_m + R_S}$$

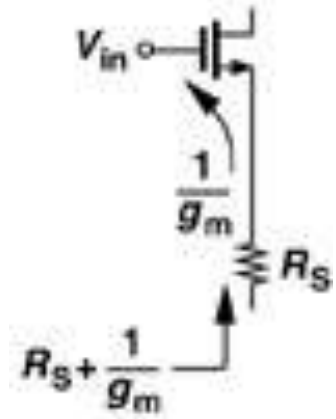Gain = $-\frac{\text{Resistance seen at the Drain}}{\text{Total Resistance in the Source Path}}$



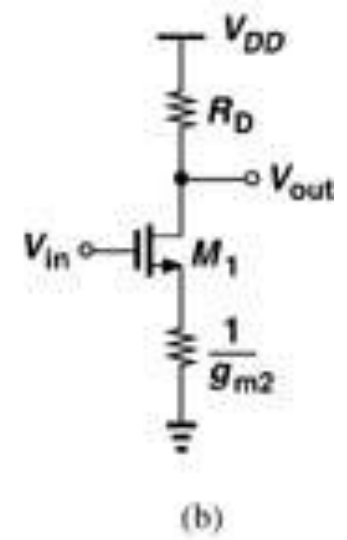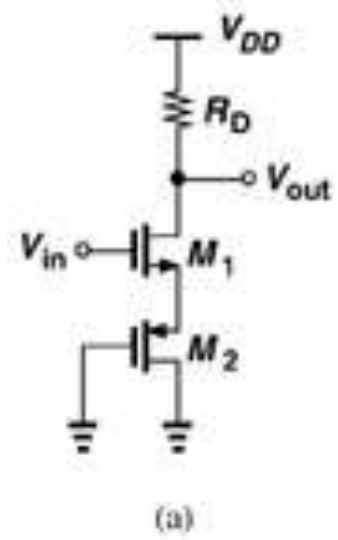Example:

$$A_v = -\frac{R_D}{1/g_{m1} + 1/g_{m2}}$$



Differential Amplifiers

- ***Single Ended and Differential Operation***
- ***Basic Differential Pair***
- ***Common-Mode Response***
- ***Differential Pair with MOS loads***

Hassan Aboushady
University of Paris VI

References

- **B. Razavi, “Design of Analog CMOS Integrated Circuits”, McGraw-Hill, 2001.**


Differential Amplifiers

- ***Single Ended and Differential Operation***
- ***Basic Differential Pair***
- ***Common-Mode Response***
- ***Differential Pair with MOS loads***

Hassan Aboushady
University of Paris VI

The concept of Half Circuit

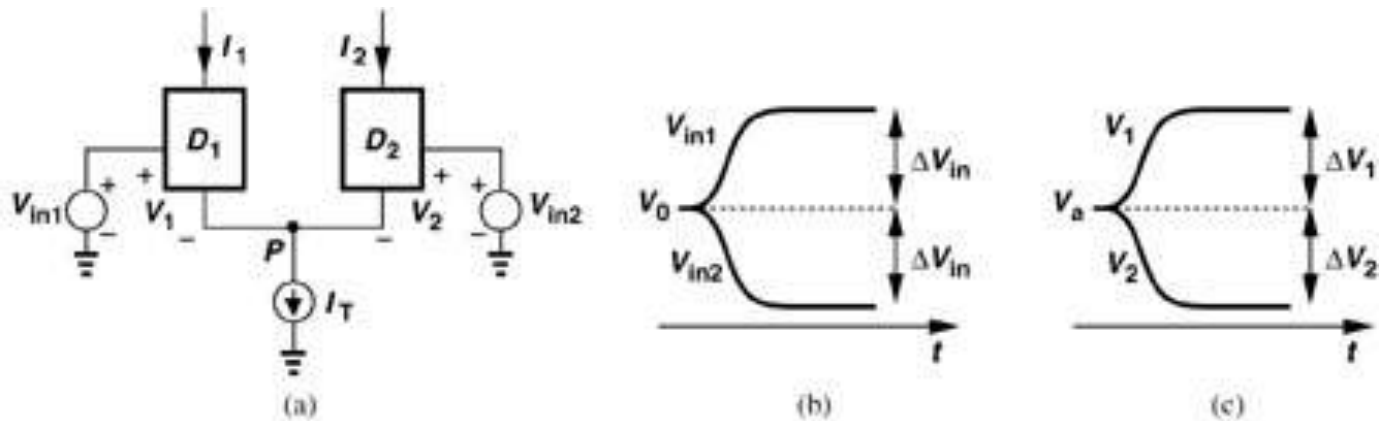
If a fully symmetric differential pair senses differential inputs then the concept of **half circuit** can be applied.



- A differential change in the inputs V_{in1} and V_{in2} is absorbed by V_1 and V_2 leaving V_p constant

Application of The Half Circuit Concept

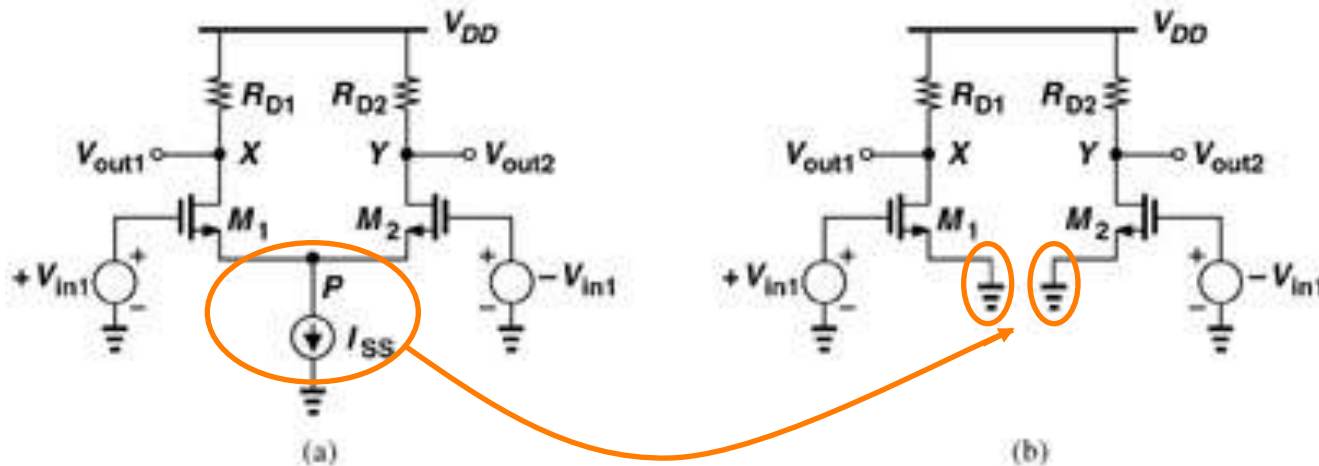Since V_P experiences no change, node P can be considered “ac ground” and the circuit can be decomposed into two separate halves



➔ **Two common source amplifiers:**


$$\frac{V_X}{V_{in1}} = -g_m R_D$$

$$\frac{V_Y}{V_{in2}} = -g_m R_D$$

$$\boxed{\frac{V_X - V_Y}{V_{in1} - V_{in2}} = -g_m R_D}$$

The Half Circuit Concept : Example

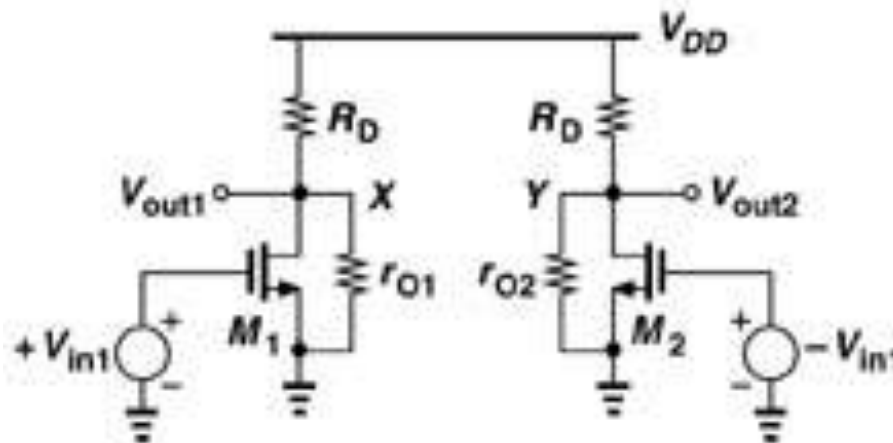Taking into account the output resistance
(channel length modulation)




➔ Two common source amplifiers:

$$\frac{V_X}{V_{in1}} = -g_m (R_D // r_{O1})$$

$$\frac{V_Y}{V_{in2}} = -g_m (R_D // r_{O2})$$

$$\frac{V_X - V_Y}{V_{in1} - V_{in2}} = -g_m (R_D // r_O)$$

Cascode Differential Pair

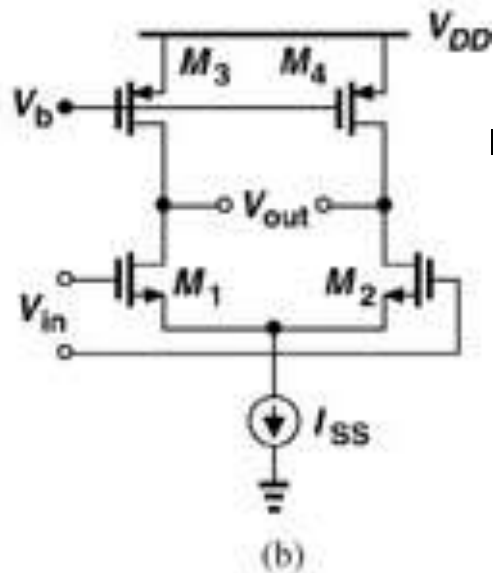

Current Source Load:



$$A_v = g_{mN} (r_{ON} \parallel r_{OP})$$

Low gain 10 to 20.

**To increase the gain:
Cascode Differential Pair**


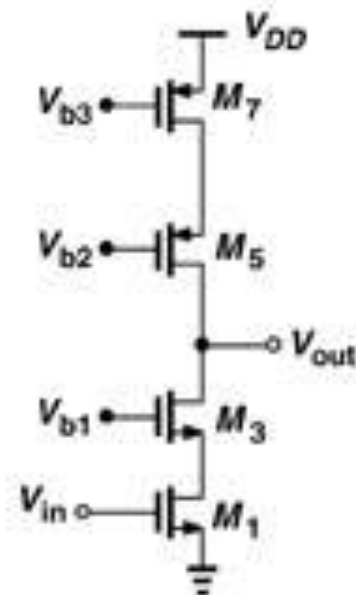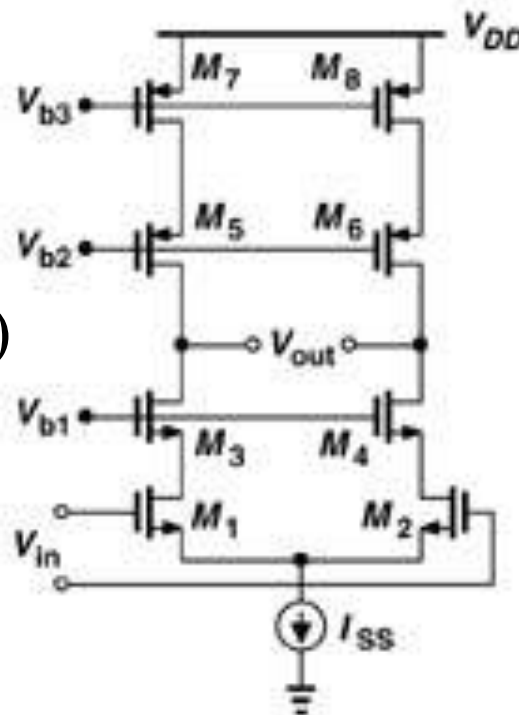
$$A_v = g_{m1} (g_{m3} r_{O3} r_{O1} \parallel g_{m5} r_{O5} r_{O7})$$



Operational Amplifiers

***Hassan Aboushady
University of Paris VI***

References


- **B. Razavi, “Design of Analog CMOS Integrated Circuits”, McGraw-Hill, 2001.**

Operational Amplifier: Performance Parameters

Gain: the open loop gain of an op-amp determines the precision of the feedback system employing the op-amp

Small Signal Bandwidth:

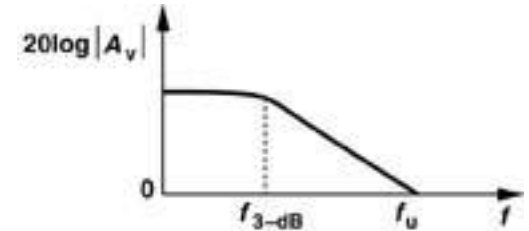Unity-Gain freq., f_u , and the 3dB freq., f_{3-dB} .



Large Signal Bandwidth (slew rate):

Op-Amp response to large transient signals.

Output Swing:


Linearity: non-linearity can be reduced by using a differential circuit and by increasing the open-loop gain in a feedback system

Noise and Offset: input noise and offset determine the minimum signal level that can be processed with reasonable quality.


Supply Rejection:

Single stage Op-Amps

Simple:

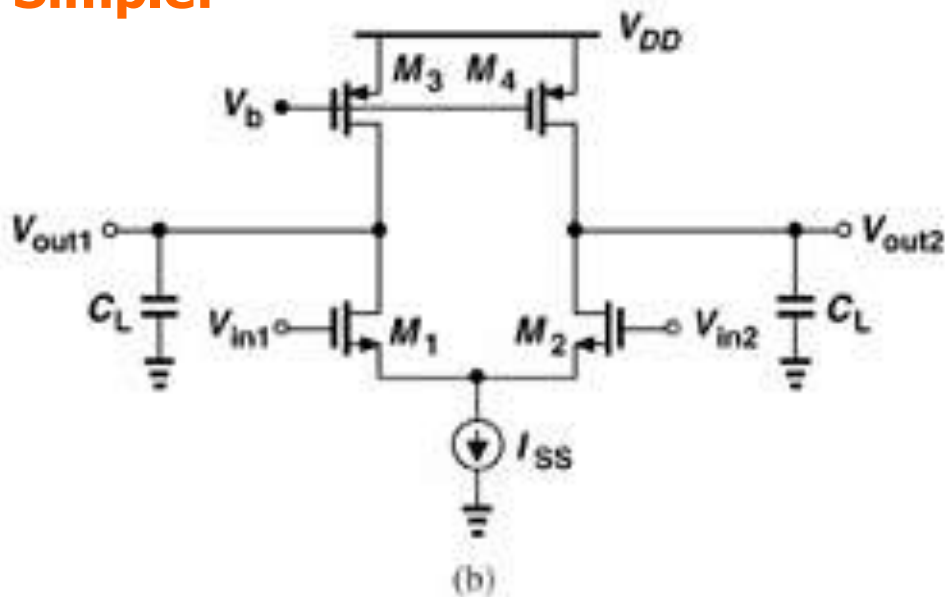

Cascode:

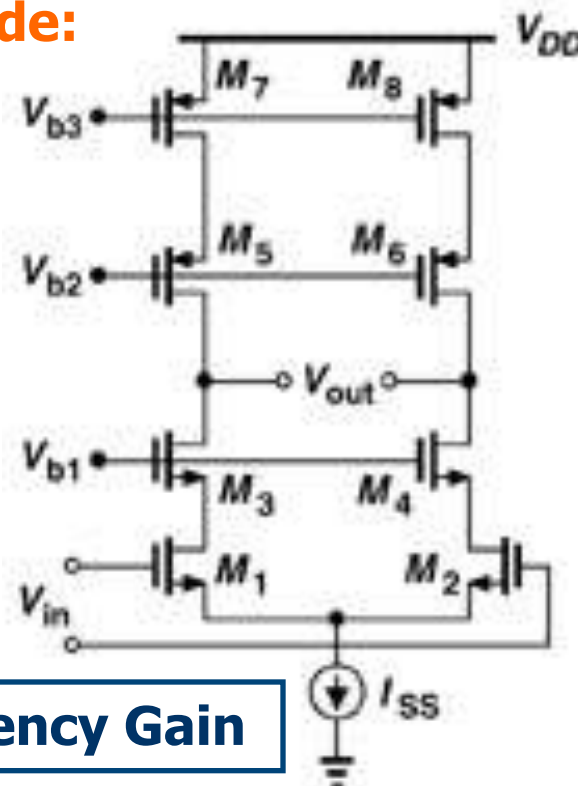

Small Signal Low Frequency Gain

$$A_0 = g_{mN} (r_{ON} // r_{OP})$$

$$A_0 \leq 20$$

$$A_0 = g_{mN} [(g_{mN} r_{ON}^2 // g_{mP} r_{OP}^2)]$$

Output Voltage Swing

$$2[V_{DD} - (V_{EG1} + V_{EG2} + V_{EGSS})]$$

$$2[V_{DD} - (V_{EG1} + V_{EG3} + V_{EG5} + V_{EG7} + V_{EGSS})]$$

Single stage Op-Amps

Example:

Design this amplifier (find all W/L as well as V_{b1} , V_{b2} and I_{ref}) with the following specifications:

$$V_{DD} = 3V$$

$$\text{Differential Output Swing} = 3V$$

$$\text{Power Dissipation} = 10mW$$

$$A_0 = 2000$$

Assume:


$$\mu_n C_{ox} = 60 \mu A / V^2$$

$$\mu_p C_{ox} = 30 \mu A / V^2$$

$$\lambda_n = 0.1 V^{-1} \quad , \quad \lambda_p = 0.2 V^{-1}$$

$$L_{eff} = 0.5 \mu m$$

$$\gamma = 0 \quad , \quad V_{THN} = |V_{THP}| = 0.7V$$

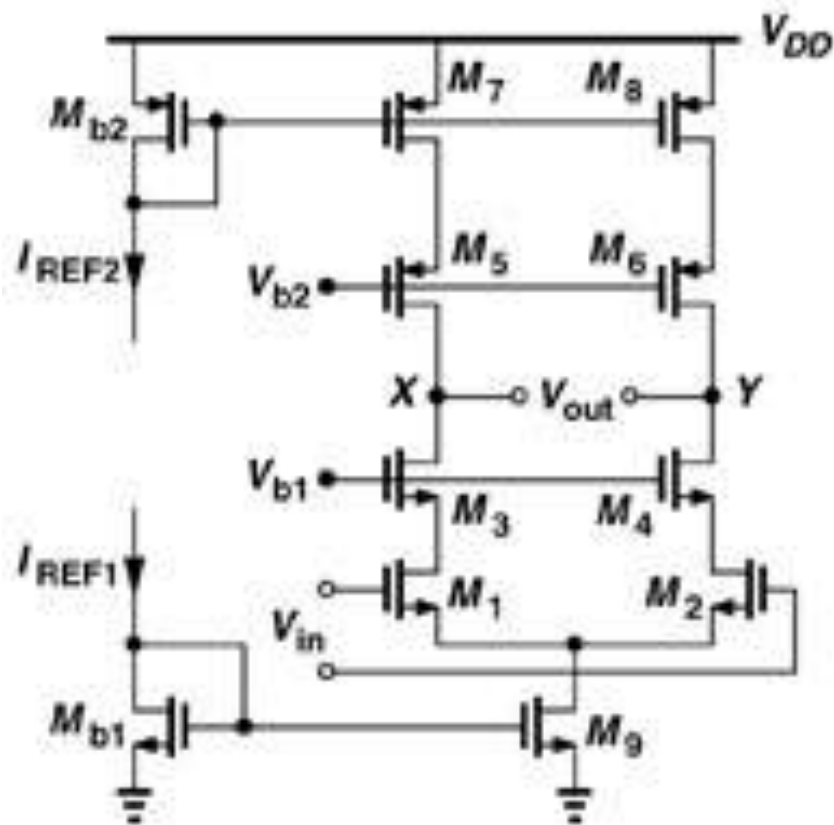

Folded Cascode Circuits

The Idea:


The input device is replaced by the opposite type.

Same Gain:


$$V_{out} = g_{m1} R_{out} V_{in}$$

Advantage:

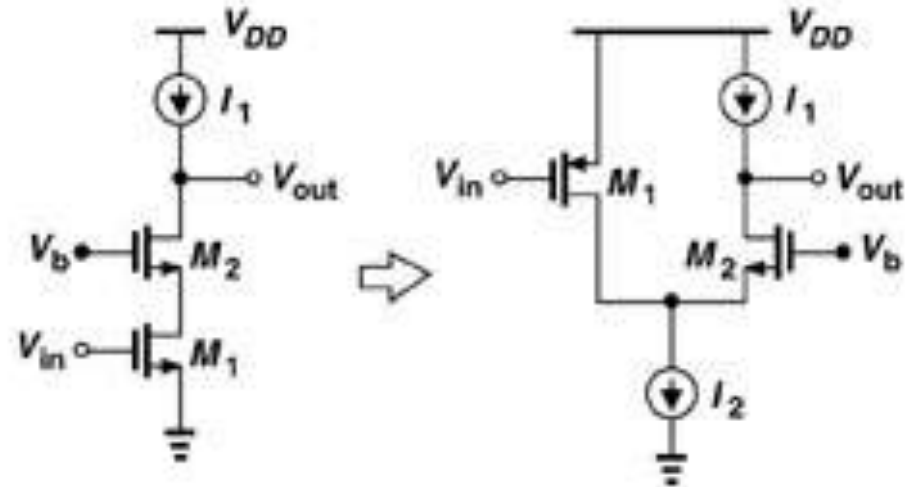More room to choose the different voltage levels.




(a)

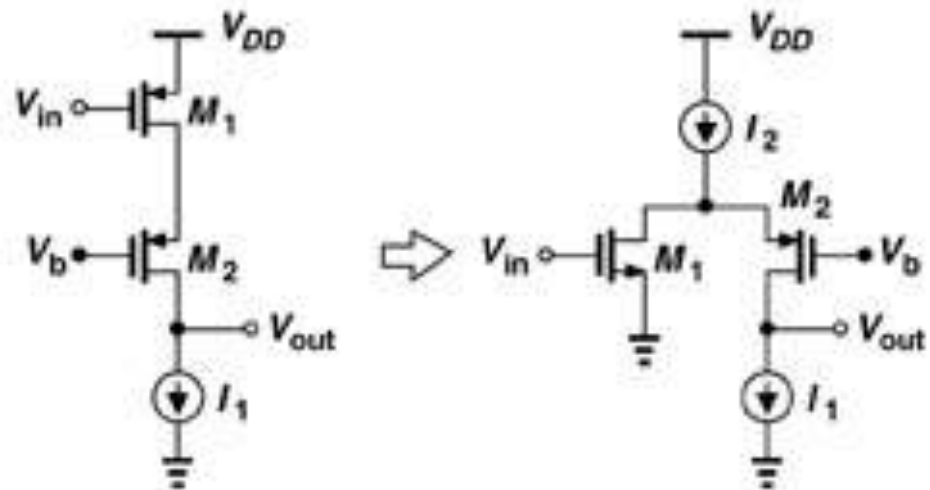


(b)

Folded Cascode Amplifier

Cascode

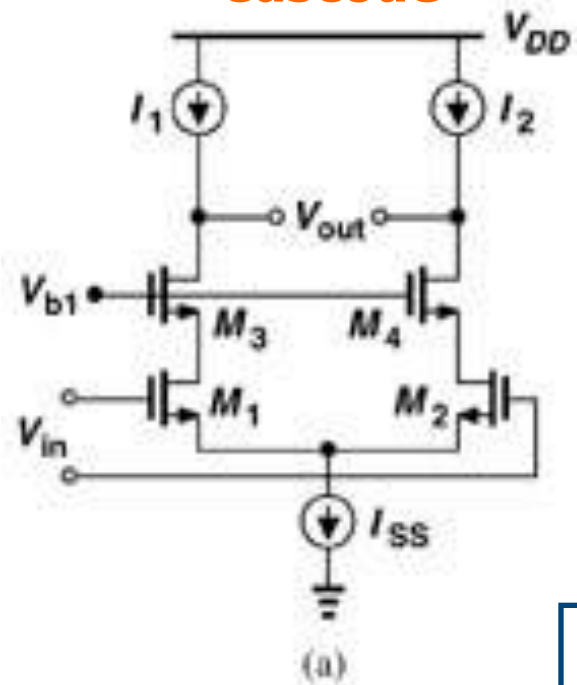

Folded Cascode

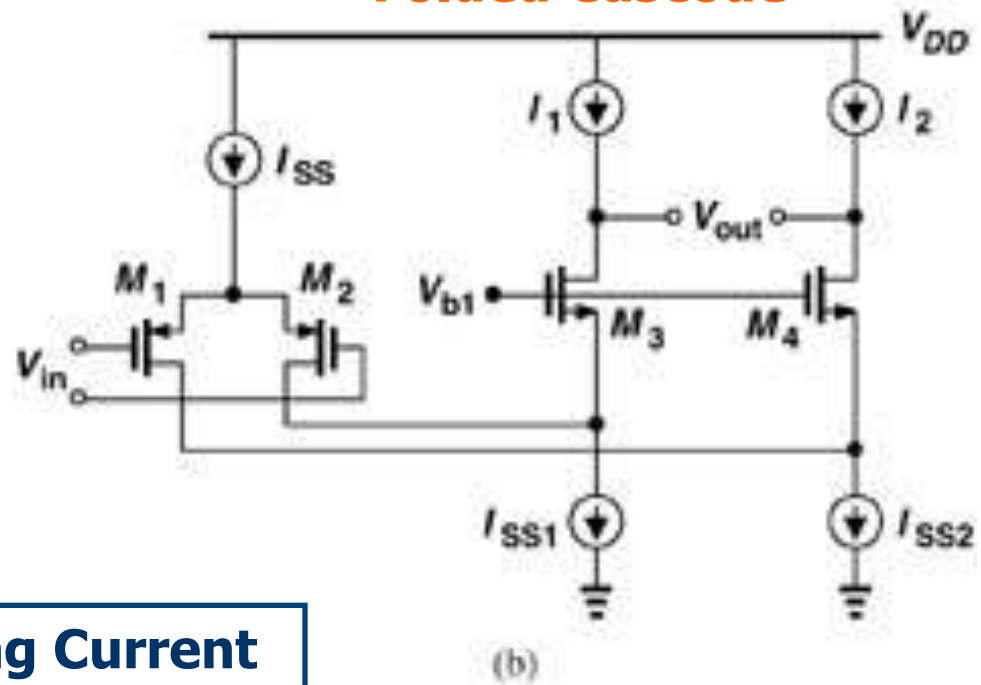

Biasing Current

$$I_{SS}$$

$$I_{SS1} = \frac{I_{SS}}{2} + I_1$$

Input Common-Mode


$$V_{in,CM} < V_{b1} - V_{GS3} + V_{TH1}$$

$$V_{in,CM} > V_{b1} - V_{GS3} + |V_{TH1}|$$

Folded Cascode Amplifier

Output Voltage Swing

$$2[V_{DD} - (V_{EG3} + V_{EG5} + |V_{EG7}| + |V_{EG9}|)]$$

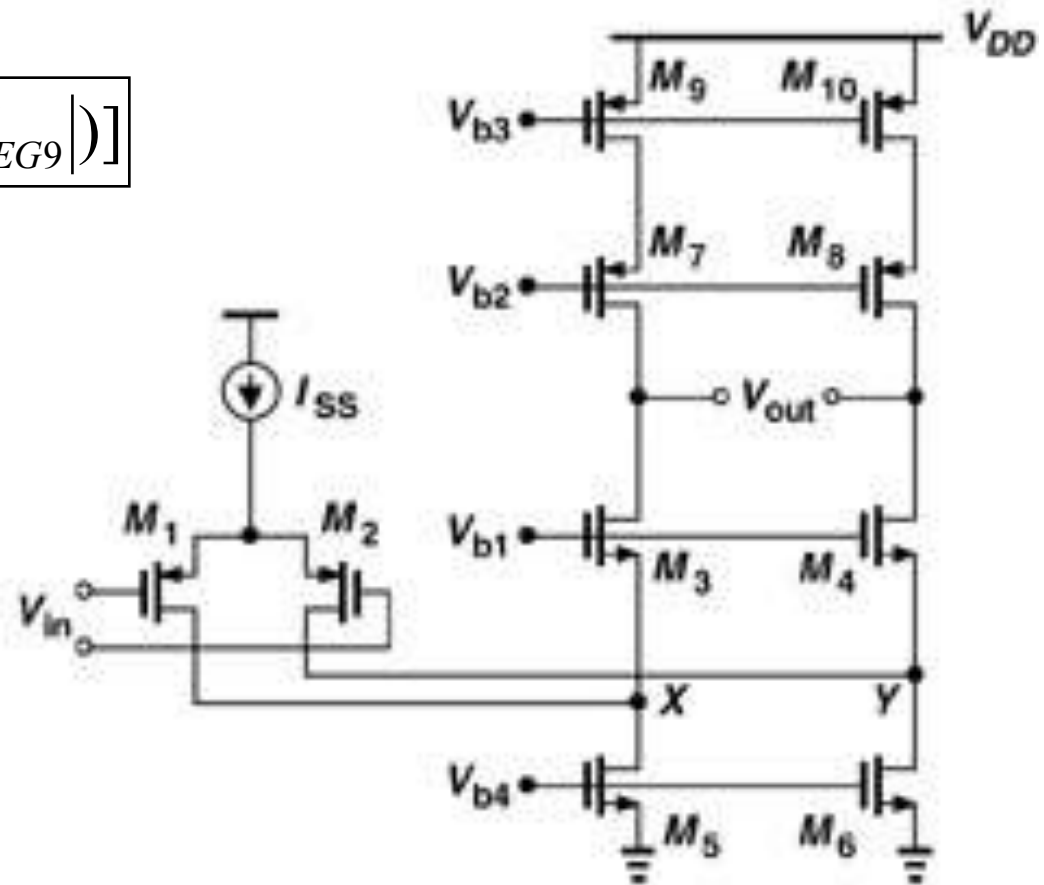


Small Signal Gain


$$A_0 \approx g_{m1} [g_{m3} r_{O3} (r_{O1} // r_{O5}) // g_{m7} r_{O7} r_{O9}]$$

Folded Cascode Amplifier

Telescopic

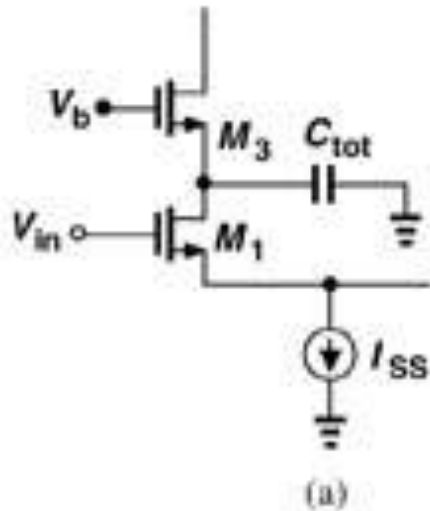

Folded Cascode


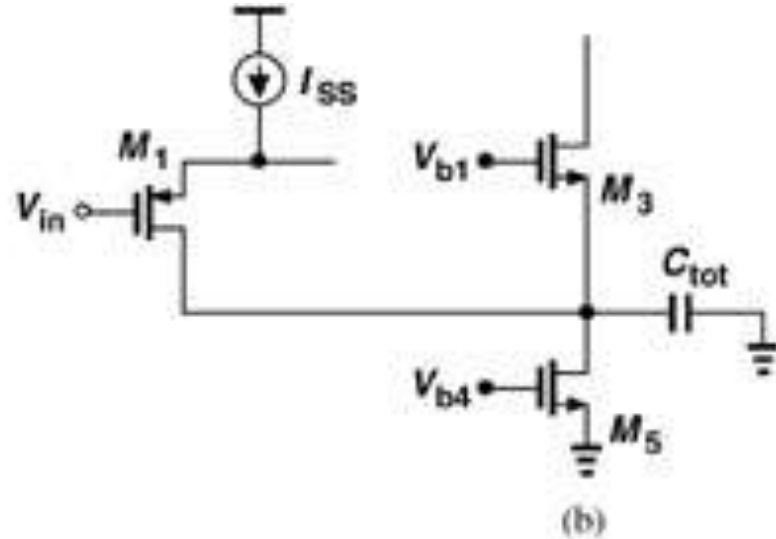


Effect of Device capacitance on the nondominant pole in telescopic and folded cascode

$$C_{tot} = C_{GS3} + C_{SB3} + C_{DB1} + C_{GD1}$$

$$C_{tot} = C_{GS3} + C_{SB3} + C_{DB1} + C_{GD1} + C_{GD5} + C_{DB5}$$

Two-Stage OpAmp

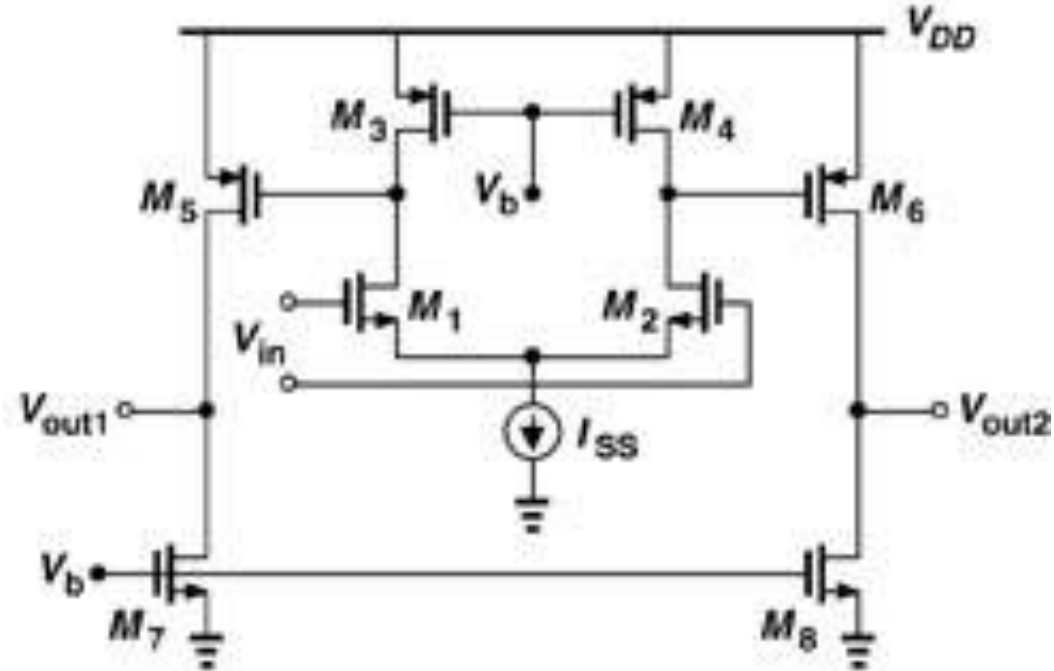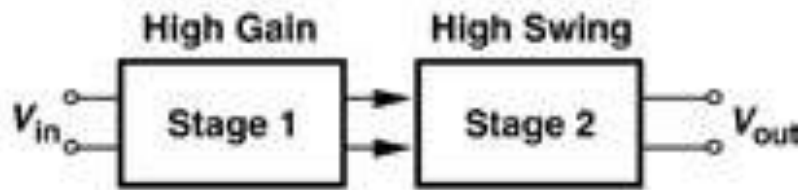

Output Voltage Swing

$$2[V_{DD} - (|V_{EG5}| + V_{EG7})]$$

Small Signal Gain

$$A_0 \approx g_{m1}(r_{O1} // r_{O3}) \times g_{m5}(r_{O5} // r_{O7})$$

Frequency Response of Amplifiers

- ***General Considerations***
 - ***Miller Effect***
 - ***Association of Poles with Nodes***
- ***Common Source Stage***
- ***Source Follower***
- ***Differential Pair***


Hassan Aboushady
University of Paris VI

References

- **B. Razavi, “Design of Analog CMOS Integrated Circuits”, McGraw-Hill, 2001.**

Miller Effect

- Miller's Theorem

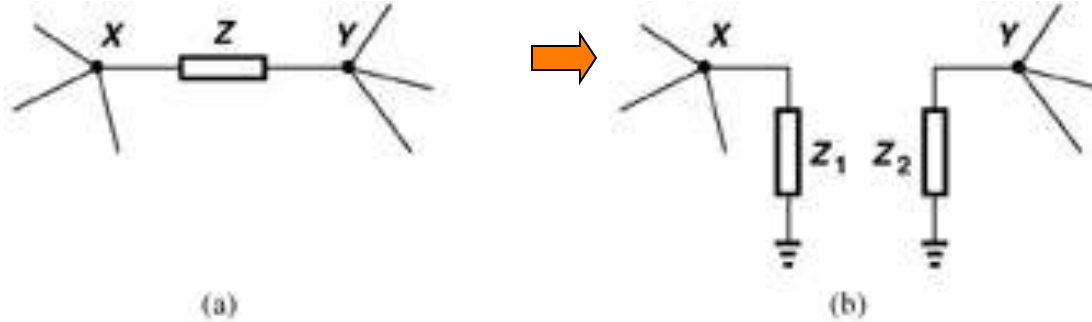

with $A_v = \frac{V_Y}{V_X}$

we have

$$Z_1 = \frac{Z}{1 - A_v}$$

$$Z_2 = \frac{Z}{1 - A_v^{-1}}$$

- Proof

$$\frac{V_X - V_Y}{Z} = \frac{V_X}{Z_1}$$



$$Z_1 = \frac{Z}{1 - \frac{V_Y}{V_X}}$$

$$\frac{V_Y - V_X}{Z} = \frac{V_Y}{Z_2}$$



$$Z_2 = \frac{Z}{1 - \frac{V_X}{V_Y}}$$

Example 1

- Calculate the input capacitance C_{in} :


$$Z = \frac{1}{sC_F} \quad Z_1 = \frac{1}{1+A}$$

→ $C_{in} = C_F(1+A)$


$A_v = \frac{V_Y}{V_X}$ should be calculated at the frequency of interest.

To simplify calculations we usually use low frequency value of A_v .

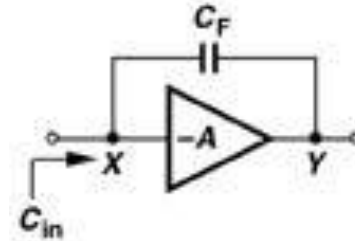Miller's theorem cannot be used simultaneously to calculate input-output transfer function and the output impedance.




(a)

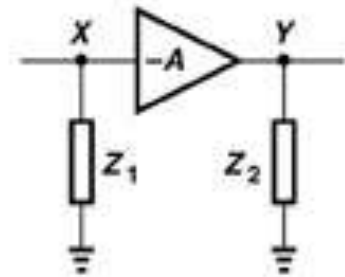

(b)

Association of Poles with Nodes

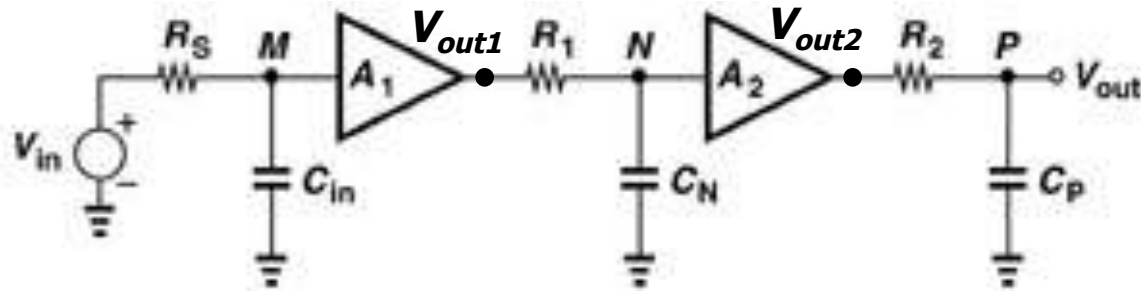

$$V_M(s) = \frac{V_{in}(s)}{R_S + \frac{1}{sC_{in}}} \frac{1}{sC_{in}} = \frac{V_{in}(s)}{1 + sR_S C_{in}}$$


$$V_N(s) = \frac{V_{out1}(s)}{1 + sR_1 C_N}$$

$$V_P(s) = \frac{V_{out2}(s)}{1 + sR_2 C_P}$$



$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_S C_{in}} \frac{A_2}{1 + sR_1 C_N} \frac{1}{1 + sR_2 C_P}$$

Association of Poles with Nodes

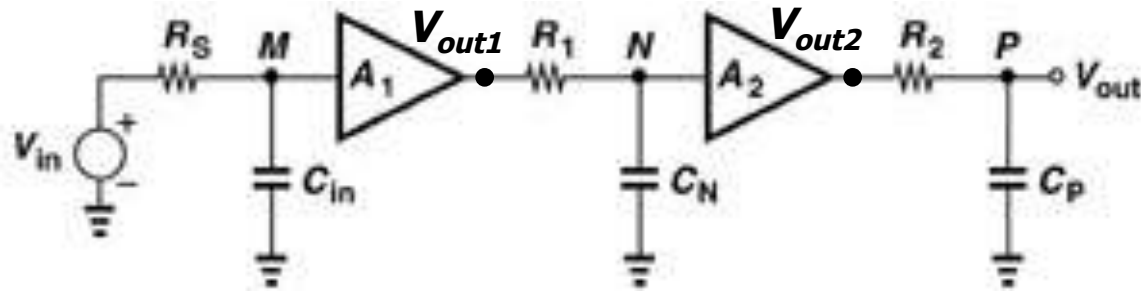

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_S C_{in}} \frac{A_2}{1 + sR_1 C_N} \frac{1}{1 + sR_2 C_P}$$

$$\omega_1 = \frac{1}{R_S C_{in}}$$

$$\omega_2 = \frac{1}{R_1 C_N}$$

$$\omega_3 = \frac{1}{R_2 C_P}$$

3 poles:

each determined by the total capacitance seen from each node to ground multiplied by the total resistance seen at the node to ground

Example 2


- Calculate the pole associated with node X:

The total equivalent capacitance seen from X to ground:

$$C_X = C_F(1 + A)$$

The pole frequency:
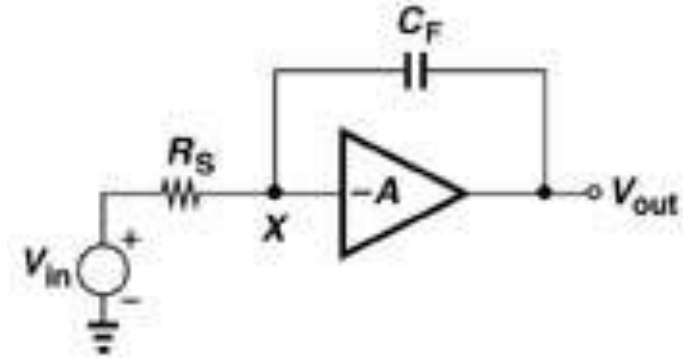
$$\omega_X = \frac{1}{R_S C_X} = \frac{1}{R_S C_F (1 + A)}$$



Common Source Stage

Neglecting channel length modulation and applying the Miller's theorem on C_{GD} , we have:

The total capacitance at node X:

$$C_X = C_{GS} + (1 - A_v)C_{GD}$$

where, $A_v = -g_m R_D$

The 1st pole frequency:


$$\omega_{p1} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})}$$

The total capacitance at the output node:

$$C_{out} = C_{DB} + (1 - A_v^{-1})C_{GD} \approx C_{DB} + C_{GD}$$

The 2nd pole frequency:

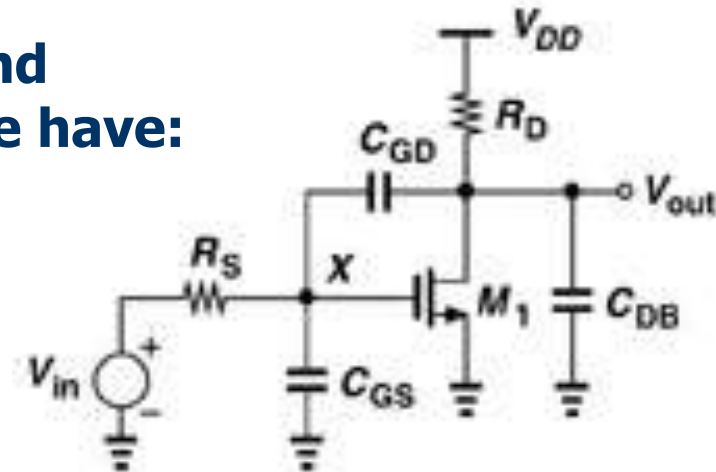
$$\omega_{p2} = \frac{1}{R_D (C_{DB} + C_{GD})}$$



Common Source Stage

The transfer function:
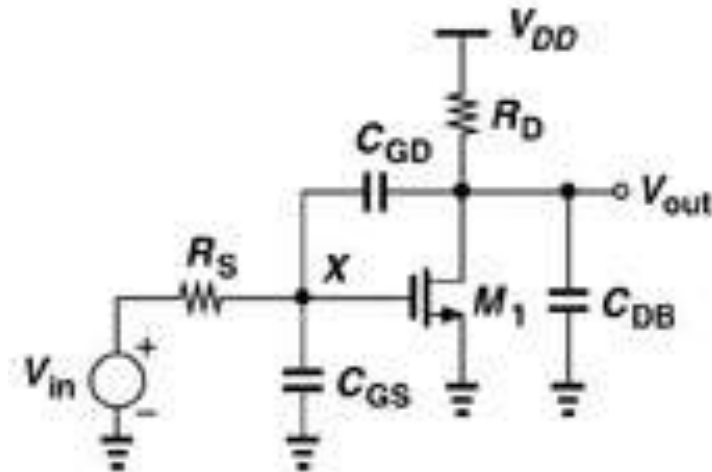
$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-g_m R_D}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$




r_o and any load capacitance can be easily included.

Sources of error (approximation):

- we have not considered the existence of zeros in the circuit
- the amplifier gain varies with frequency

Common Source : “exact “ Transfer Function

To obtain the exact transfer function:

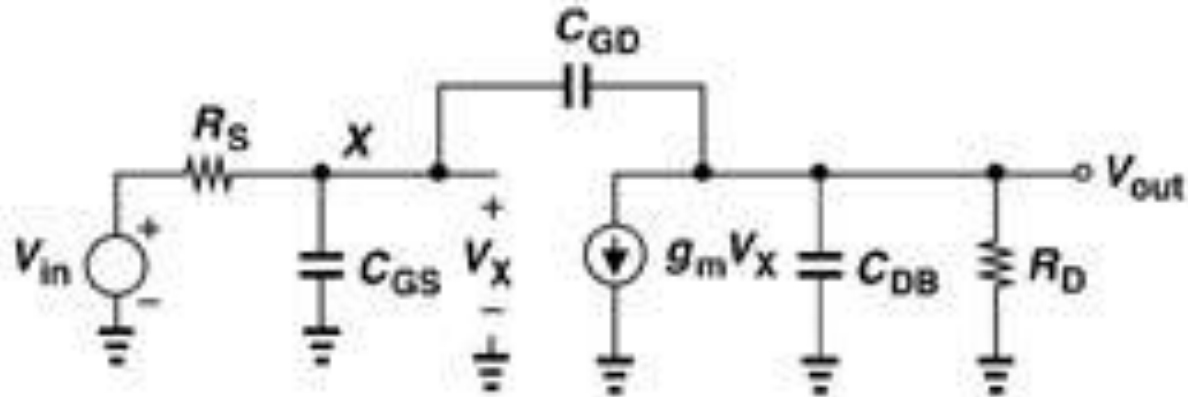

Applying Kirchoff Current Law (KCL):

$$\frac{V_X - V_{in}}{R_S} + sC_{GS}V_X + sC_{GD}(V_X - V_{out}) = 0$$

$$sC_{GD}(V_{out} - V_X) + g_m V_X + \left(sC_{DB} + \frac{1}{R_D} \right) V_{out} = 0$$

Common Source : "exact" 1st pole

After some manipulations, we get:

$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

with $\xi = C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB}$

Writing the denominator as: $D = \left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$

Assuming $|\omega_{p1}| \ll |\omega_{p2}|$

→ $\omega_{p1} \approx \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$

Compare this result with ω_{in} calculated using Miller's Theorem

Common Source : "exact" 2nd pole


$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D \xi s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

with $\xi = C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB}$

having $D = \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1$

and $\omega_{p1} \approx \frac{1}{R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}$

then $\omega_{p2} = \frac{1}{R_S R_D \xi} \frac{1}{\omega_{p1}}$

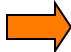 $\omega_{p2} = \frac{R_S(1 + g_m R_D)C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})}{R_S R_D (C_{GS}C_{GD} + C_{GS}C_{DB} + C_{GD}C_{DB})}$

Comparison between “exact” and Miller’s theorem

1st pole:

If

$$R_D (C_{GD} + C_{DB})$$

is negligible

exact

$$\omega_{p1} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD}) + R_D (C_{GD} + C_{DB})}$$

Miller

$$\omega_{p1} = \frac{1}{R_S (C_{GS} + (1 + g_m R_D) C_{GD})}$$

2nd pole:

exact

$$\omega_{p2} = \frac{R_S (1 + g_m R_D) C_{GD} + R_S C_{GS} + R_D (C_{GD} + C_{DB})}{R_S R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

if $C_{GS} \gg (1 + g_m R_D) C_{GD} + \frac{R_D}{R_S} (C_{GD} + C_{DB})$

$$\omega_{p2} \approx \frac{C_{GS}}{R_D (C_{GS} C_{GD} + C_{GS} C_{DB} + C_{GD} C_{DB})}$$

Miller



$$\omega_{p2} = \frac{1}{R_D (C_{DB} + C_{GD})}$$

Common Source : transfer function zero

After some manipulations, we get:


$$\frac{V_{out}}{V_{in}} = \frac{(sC_{GD} - g_m)R_D}{R_S R_D s^2 + [R_S(1 + g_m R_D)C_{GD} + R_S C_{GD} + R_S C_{GS} + R_D(C_{GD} + C_{DB})]s + 1}$$

$$\omega_z = \frac{g_m}{C_{GD}}$$

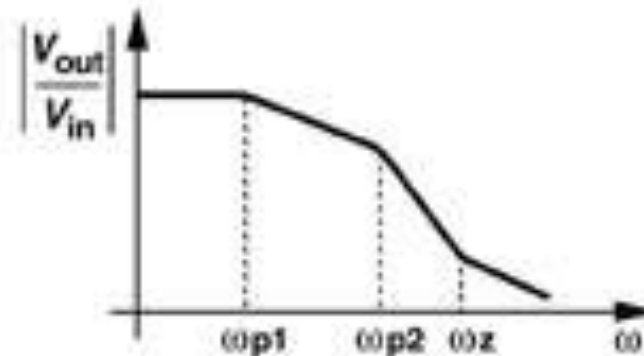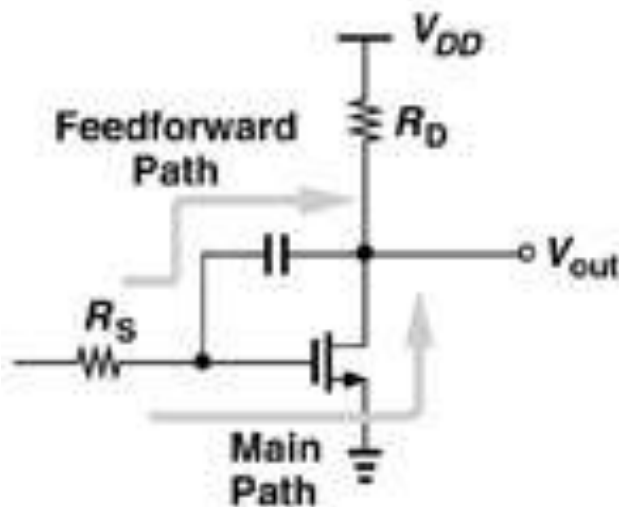


Stability and Frequency Compensation
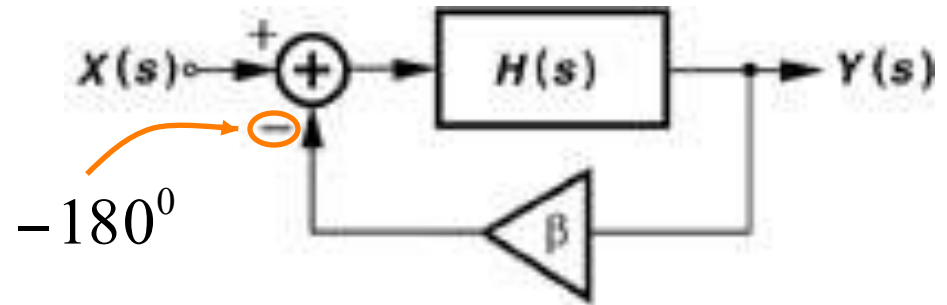
$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$




Condition for oscillations

$$\beta H(j\omega) = -1 \begin{cases} |\beta H(j\omega)| = 1 \\ \angle \beta H(j\omega) = -180^\circ \end{cases}$$

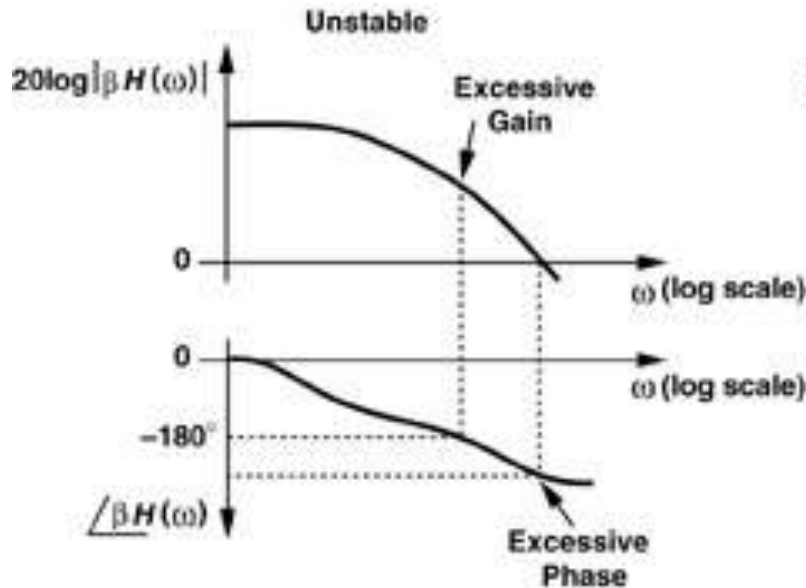

(a)

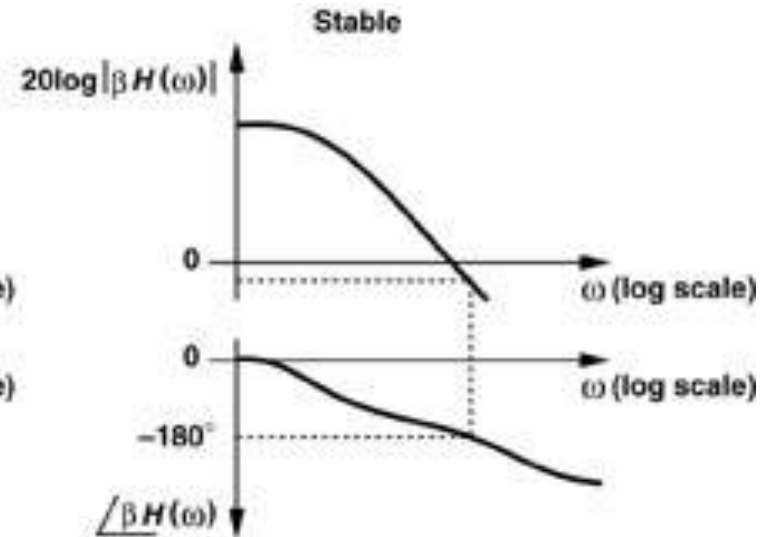

(b)

Bode Plot & Root Locus


Bode Plot:

(1) The slope of the magnitude plot changes by + 20 dB/dec at every zero frequency

- 20 dB/dec at every pole frequency

(2) For a pole (zero) frequency of ω_m , the phase begins to fall (rise) at $0.1\omega_m$, experiences a change - 45° (+ 45°) at ω_m , and a change of -90° (+ 90°) at $10\omega_m$.

Root Locus: $s_p = \sigma_p + j\omega_p$

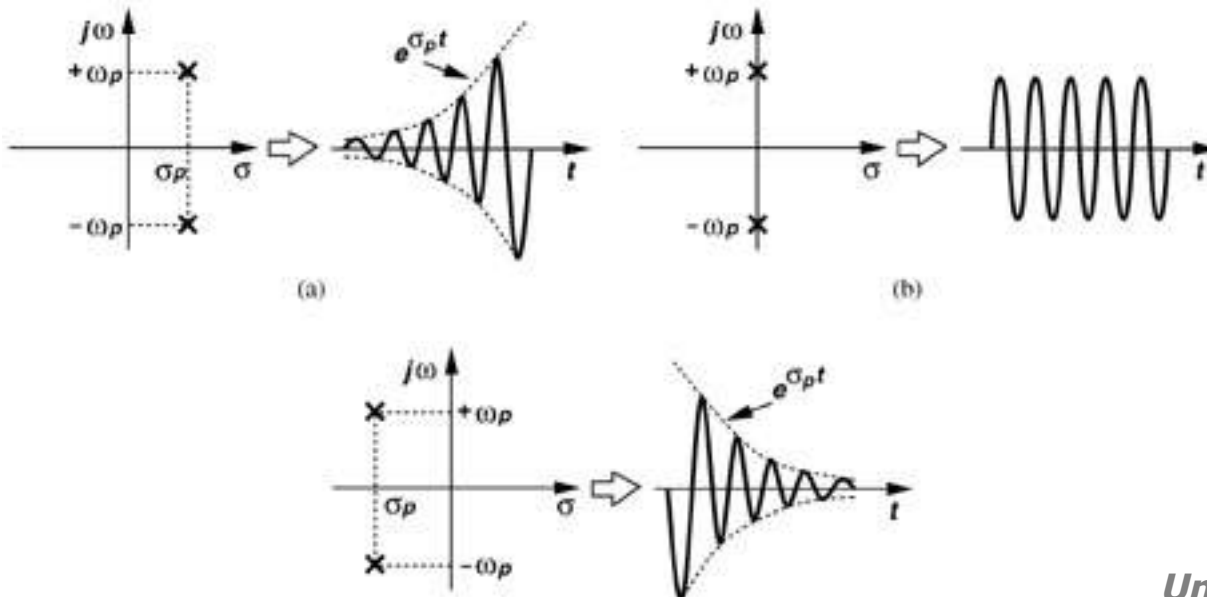


One-Pole System

$$H(s) = \frac{A_0}{1 + s / \omega_0}$$

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$

Bode Plot:

We plot $|\beta H(s)|$
and $\angle \beta H(s)$ at $s=j\omega$

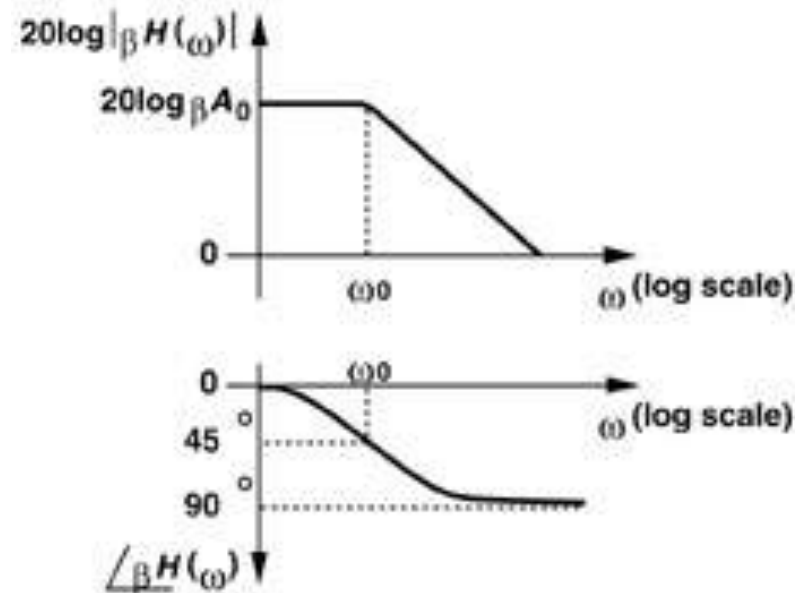


A single pole cannot contribute to a phase shift greater than 90°
 → the system is unconditionally stable.

Root Locus:


$$s_p = -\omega_0(1 + \beta A_0)$$

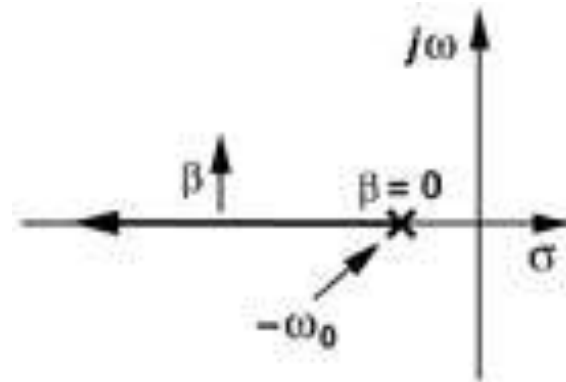We plot the location of the poles
as the loop gain varies



Two-Pole System

Bode Plot:

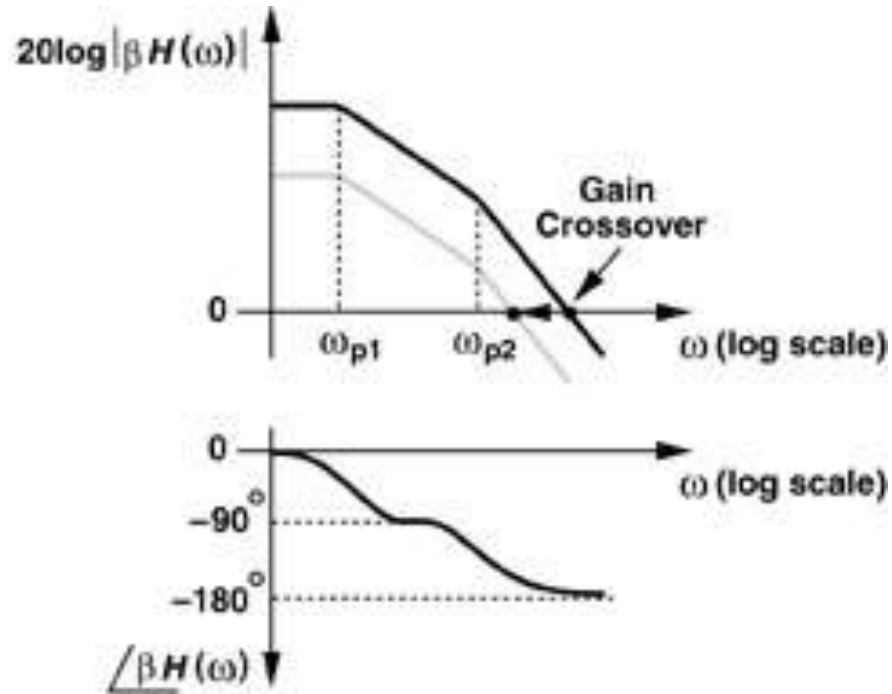

$\beta \downarrow \Rightarrow$ Gain \downarrow

\Rightarrow No Phase Change

\Rightarrow More Stable System

Two-Pole System

Root Locus:

$$H(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$\frac{Y(s)}{X(s)} = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) + \beta A_0}$$


$$= \frac{A_0 \omega_{p1} \omega_{p2}}{s^2 + (\omega_{p1} + \omega_{p2})s + (1 + \beta A_0) \omega_{p1} \omega_{p2}}$$

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$

$$s_{1,2} = -\frac{1}{2}(\omega_{p1} + \omega_{p2}) \pm \frac{1}{2} \sqrt{(\omega_{p1} + \omega_{p2})^2 - 4(1 + \beta A_0) \omega_{p1} \omega_{p2}}$$


For $\beta = 0$ \Rightarrow $s_{1,2} = -\omega_{p1}, -\omega_{p2}$
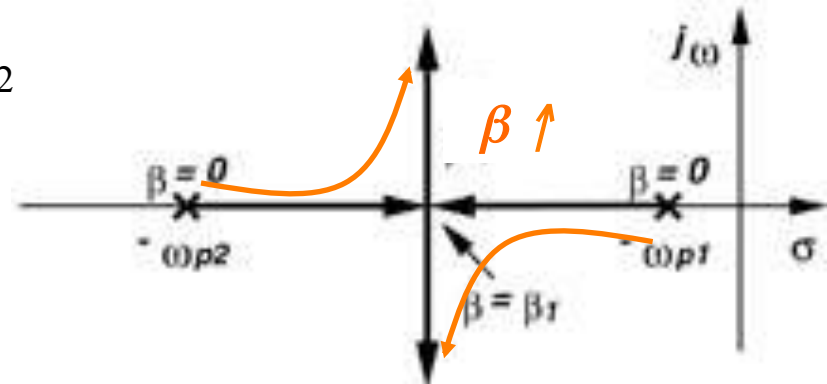
$$\beta_1 = -\frac{1}{A_0} \frac{(\omega_{p1} - \omega_{p2})^2}{4 \omega_{p1} \omega_{p2}}$$



Three-Pole System

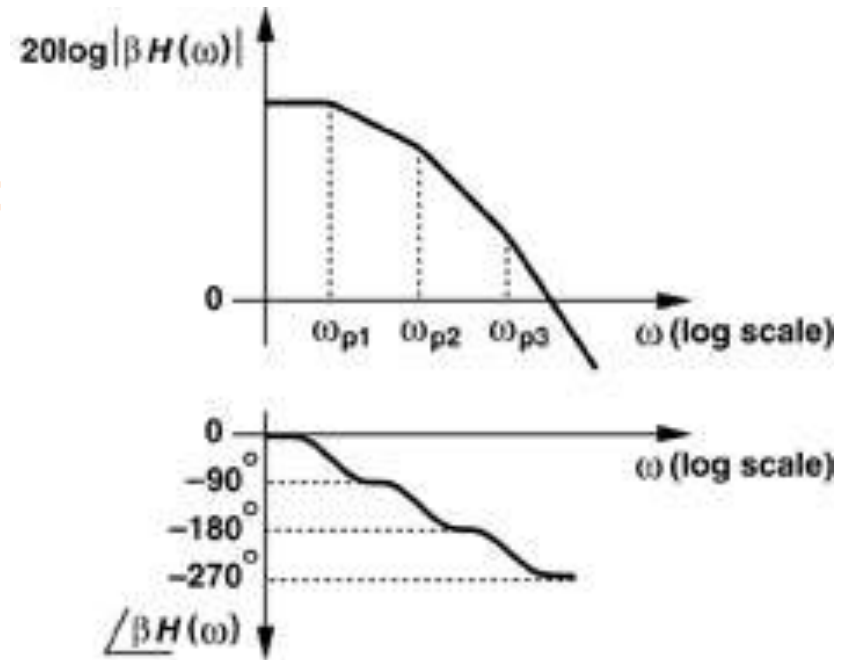Additional poles and zeros impact the phase much more than the magnitude




Phase Margin

To ensure stability $|\beta H(s)|$ must drop to unity before $\angle \beta H(s)$ crosses -180° .


How far should PX be from GX ?

GX: Gain Crossover
PX: Phase Crossover

Small Phase margin

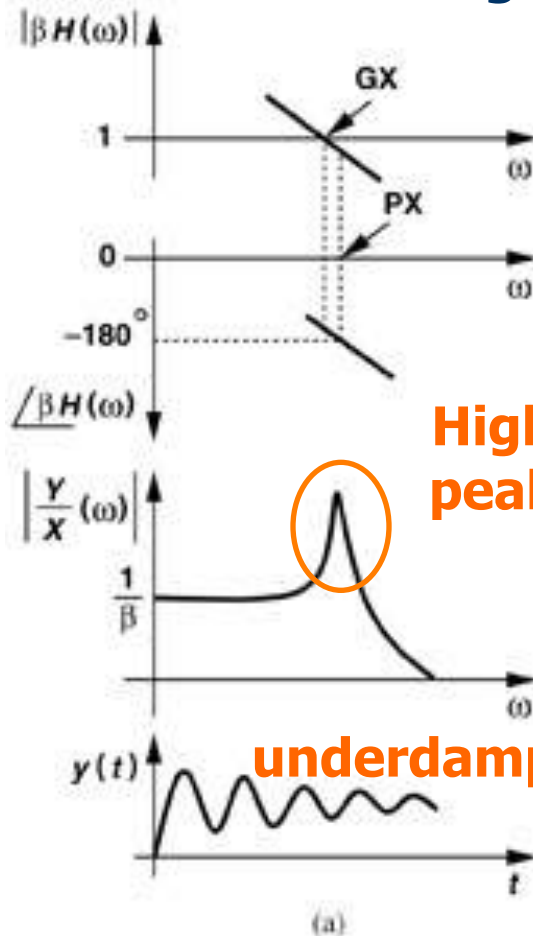

High Phase margin

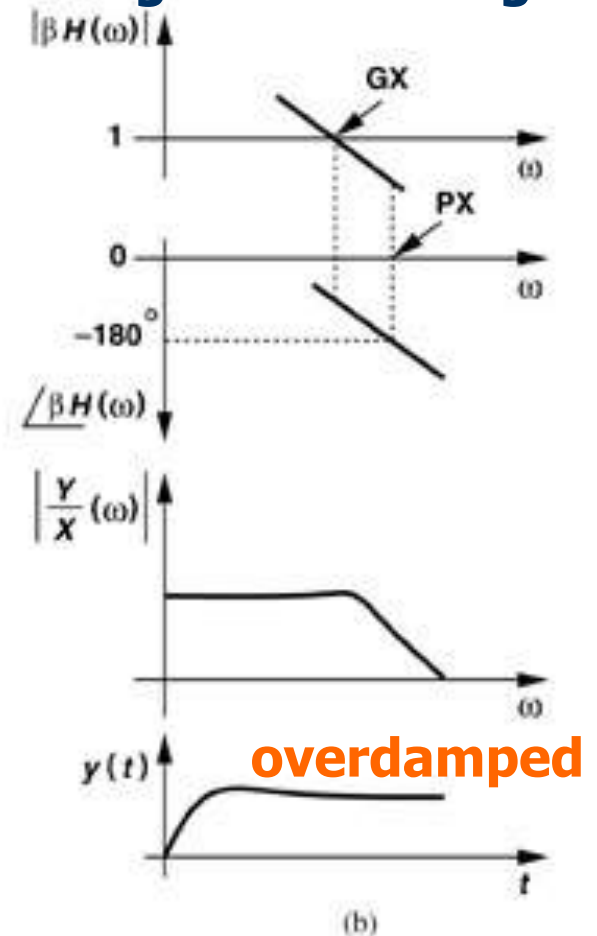


Frequency Response:

Step Response:

Example

A two-pole feedback system is designed such that $|\beta H(\omega_{p2})| = 1$ and $|\omega_{p1}| \ll |\omega_{p2}|$. **What is the phase margin ?**

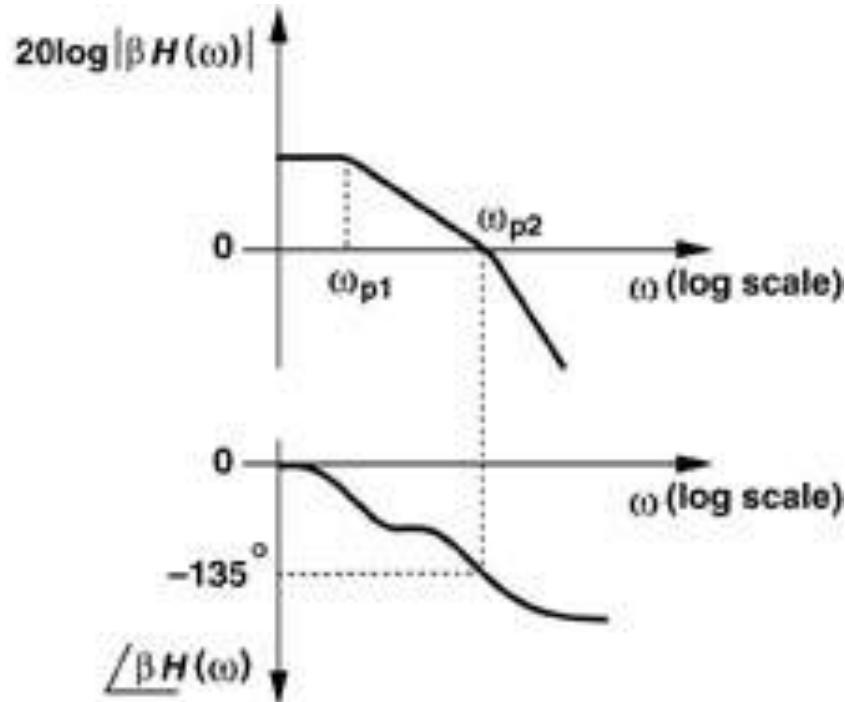

Since $\angle \beta H(s)$ reaches -135° at $\omega = \omega_{p2}$

➔ The phase margin is equal to 45° .





How much phase margin is adequate ?

For $PM=45^\circ \rightarrow \beta H(\omega_1) = 1 \times \exp(-j135)$

$$\left. \frac{Y(s)}{X(s)} \right|_{s=j\omega_1} = \frac{1}{\beta} \frac{1 \times \exp(-j135^\circ)}{1 + 1 \times \exp(-j135^\circ)}$$

$$\left. \frac{Y(s)}{X(s)} \right|_{s=j\omega_1} = \frac{1}{\beta} \frac{-\sqrt{2}/2 - j\sqrt{2}/2}{1 - \sqrt{2}/2 - j\sqrt{2}/2}$$


$$\left| \left. \frac{Y(s)}{X(s)} \right|_{s=j\omega_1} \right| = \frac{1.3}{\beta}$$

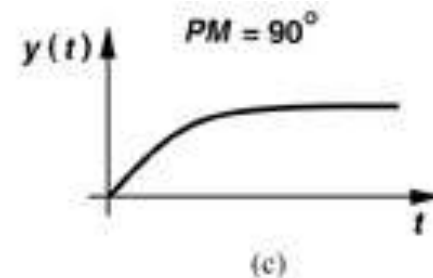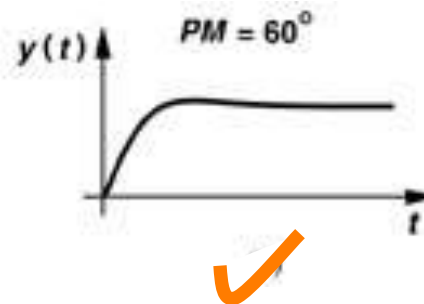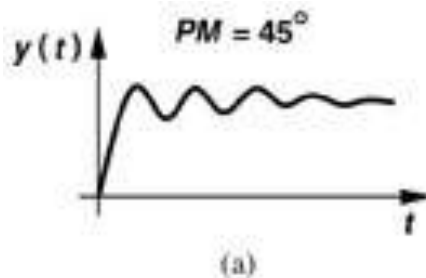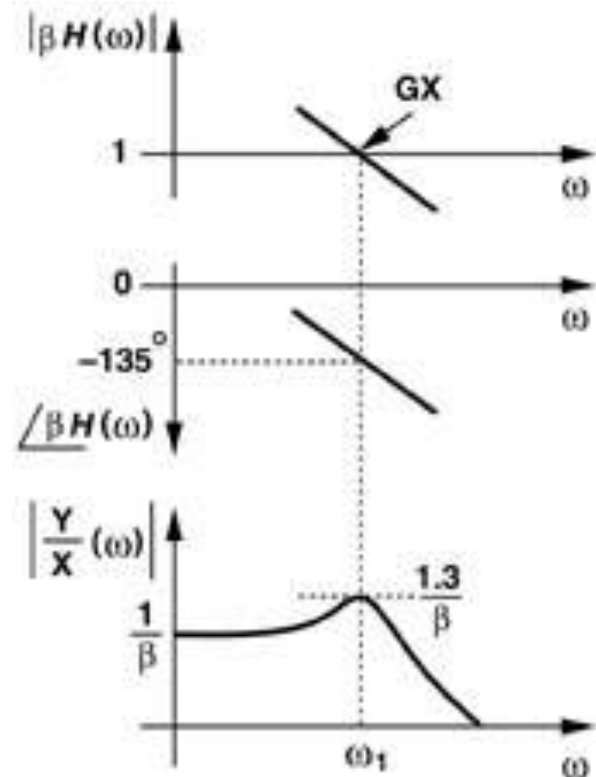

Frequency Compensation

Solution 1


➔ **Modify** $\angle \beta H(s)$

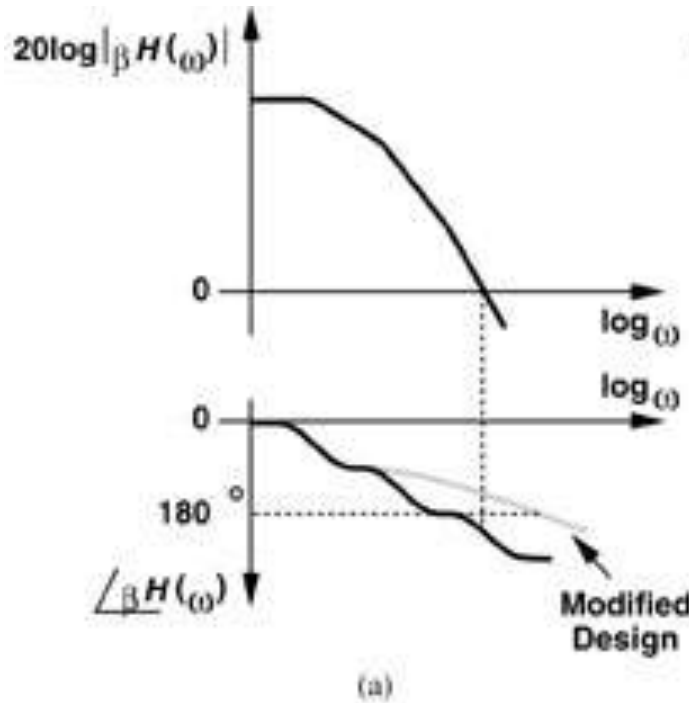

➔ **Poles** $\downarrow \Rightarrow$ **Stages** $\downarrow \Rightarrow$ **Gain** \downarrow

Solution 2

➔ **Modify** $|\beta H(s)|$

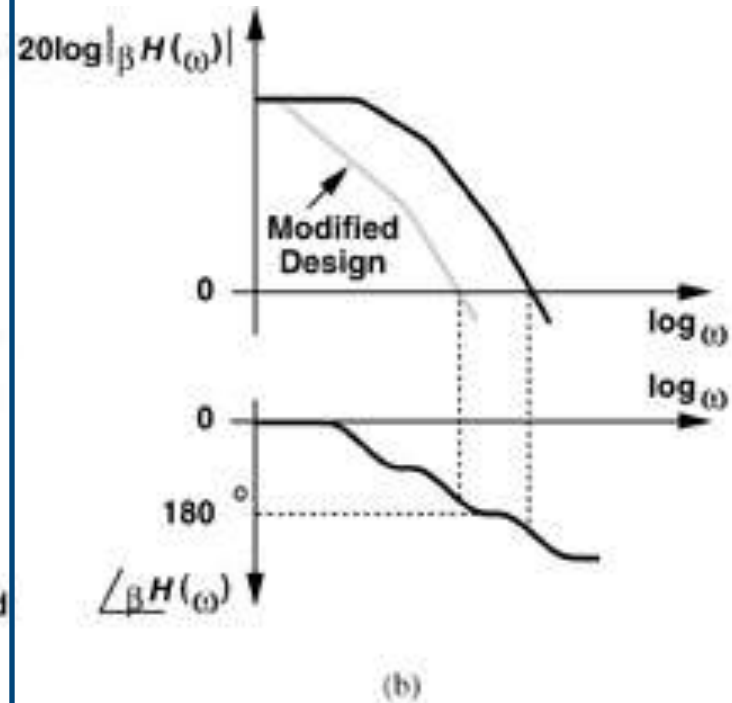

➔ **Reduces bandwidth**

Frequency Compensation



Frequency Compensation:

- lower the frequency of the dominant pole
 → increase the load capacitance

How much $\omega_{p,out}$ must be shifted down ?

Assume:

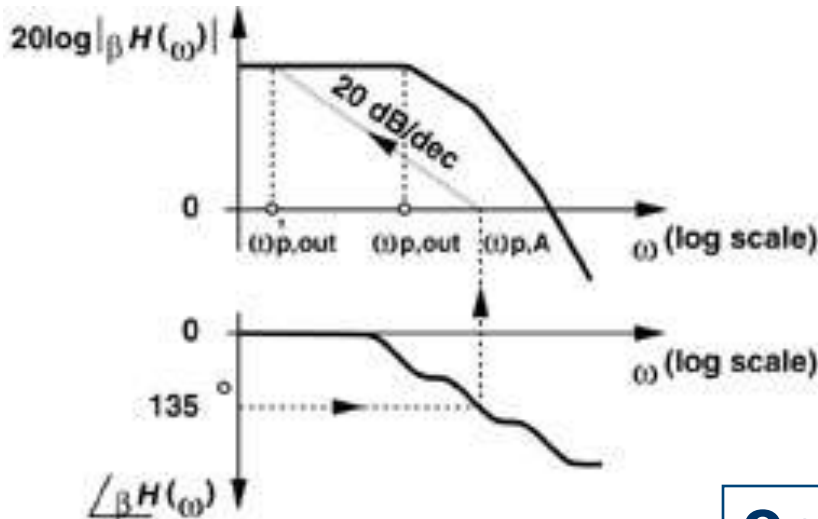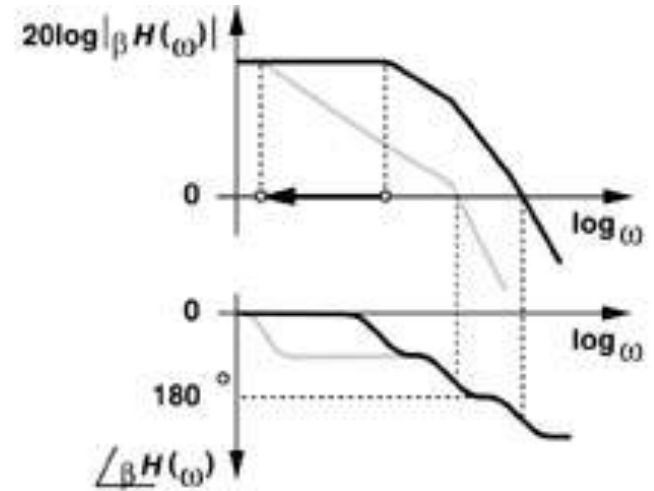- 1- $\omega_{p,A} \ll \omega_{p,N}$ → $\angle \beta H(\omega_{p,A}) = 135^\circ$
- 2- required PM = 45°



→ -The new dominant pole: $\omega'_{p,out}$

-The load capacitance must be increased by a factor $\omega_{p,out} / \omega'_{p,out}$


Op-Amp GBW = 1st non dominant pole

Is it possible to compensate using R_{out} ?




Although,

$$\omega_{p,out} = \frac{1}{R_{out} C_L}$$

The answer is **NO !**

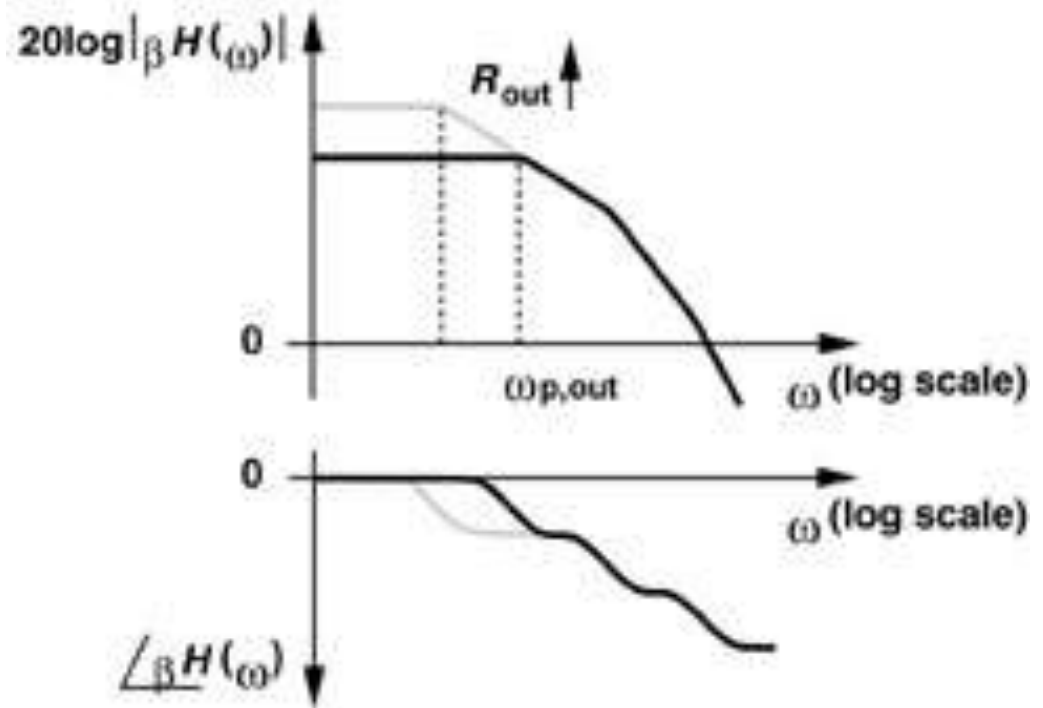

Compensation of 2 stage Op-Amps

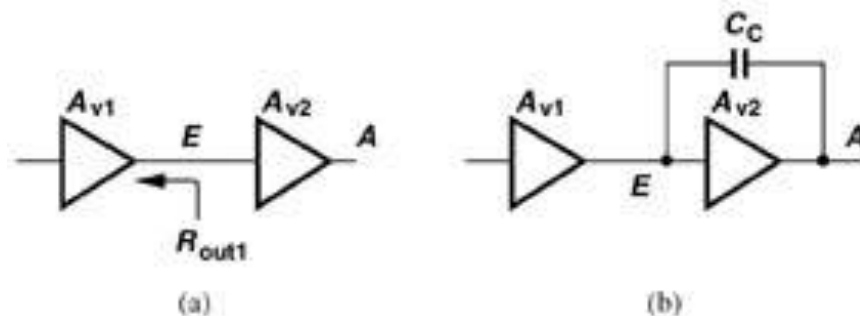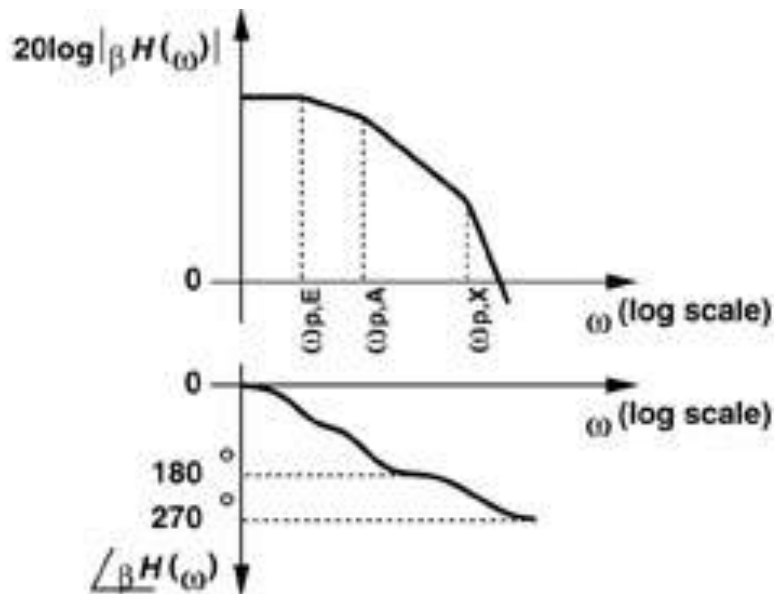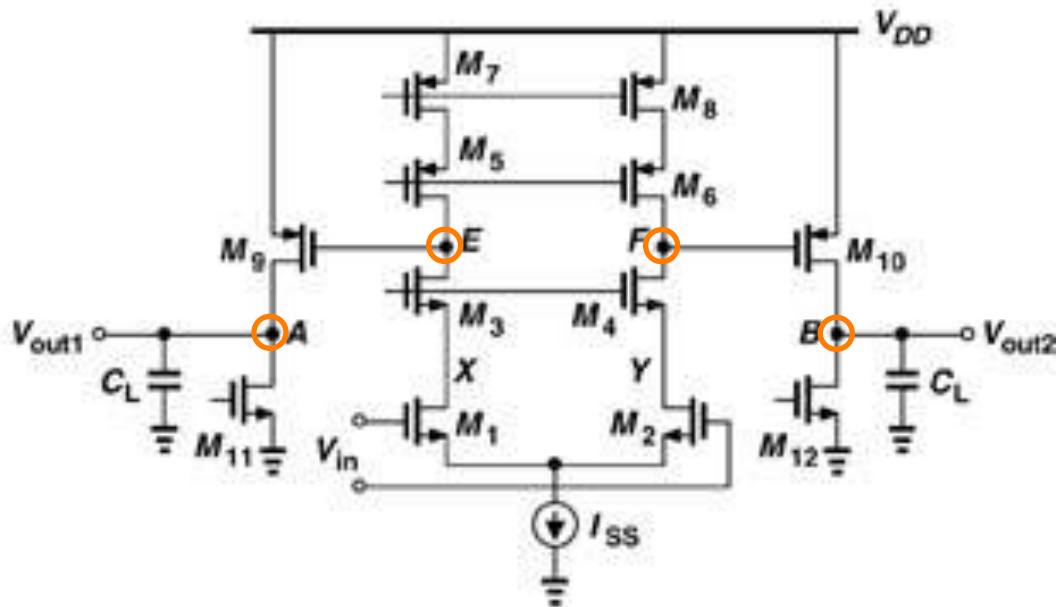


Total capacitance at node E:

$$C_E + (1 + A_{v2})C_C$$

2nd Stage

➔ Common Source Amplifier:


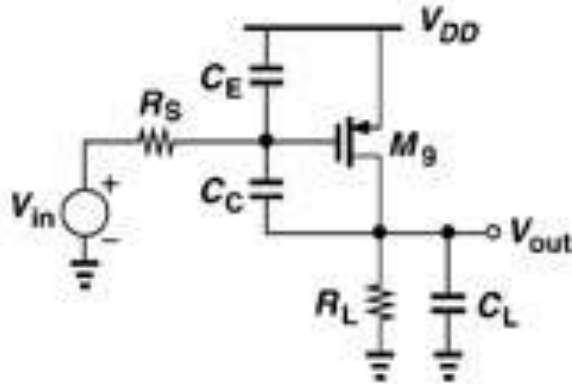


$$\omega_{p1} \approx \frac{1}{R_S \left[(1 + g_{m9} R_L) (C_C + C_{GD9}) + C_E \right] + R_L (C_C + C_{GD9} + C_L)}$$

$$\omega_{p2} = \frac{R_S \left[(1 + g_{m9} R_L) (C_C + C_{GD9}) + C_E \right] + R_S C_{GS} + R_L (C_C + C_{GD9} + C_L)}{R_S R_L \left[(C_C + C_{GD9}) C_E + (C_C + C_{GD9}) C_L + C_E C_L \right]}$$

Pole Splitting

Common Source Amplifier:

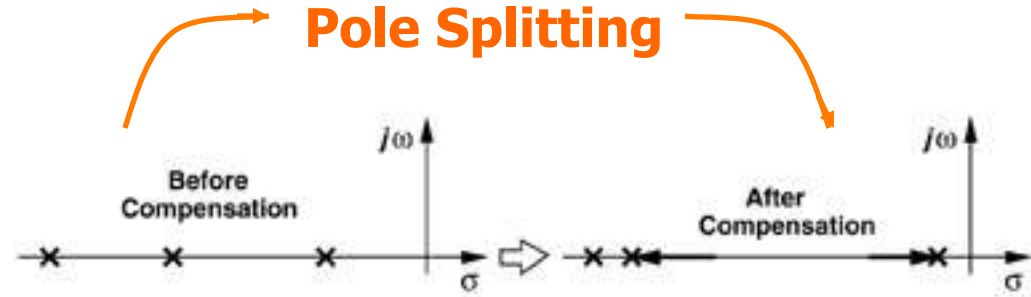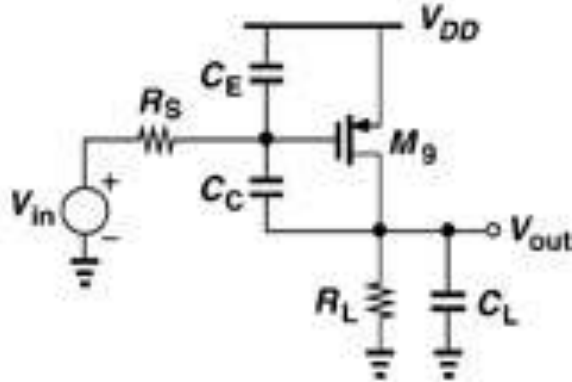

Before compensation:

$$\omega_{p1} \approx \frac{1}{R_S (C_E + (1 + g_{m9} R_L) C_{GD9})}$$

$$\omega_{p2} \approx \frac{1}{R_L C_L}$$

After compensation:

$$\omega_{p1} \approx \frac{1}{R_S [C_E + (1 + g_{m9} R_L) (C_C + C_{GD9})]}$$

$$\omega_{p2} \approx \frac{g_{m9}}{C_E + C_L}$$